



Lab 11

Display Student ID & Birthday

Prof. Chih-Cheng Tseng (曾志成)

cctseng@mail.ntou.edu.tw

Contents of this slide are provided by NTOU VLSI Lab601

Objectives


- Display Student ID
- Display Birthday

LAB 1 – Display Student ID (1/5)

- Design a Finite State Machine (FSM) that outputs digits of an encoded student ID one by one.
- Rules to encode the student ID
 - When a repeated digit is encountered, replace the first occurrence with 'A', the next with 'B', and so on.
 - The last occurrence of each repeated digit remains unchanged.
 - For example, 00957001 becomes **A**B957**C**01.
 - When there are multiple sets of repeated digits in the student ID, replace the repeated digits with letters A ~ F in the order they appear.
 - For example, 00957007 becomes **A**B95**C****D**07.
 - When there are letters already present in the student ID, skip the original letters.
 - For example, 0086B002 becomes **A****C**86**B****D**02.


LAB 1 – Display Student ID (2/5)

- Signal settings
 - Input: clk and reset
 - Output: student_id[3:0]
- State diagram: Assume 01057086 → A1B57086

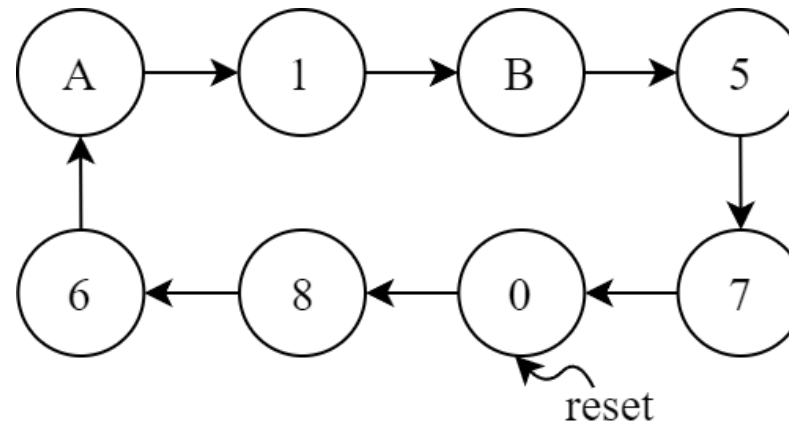

LAB 1 – Display Student ID (3/5)

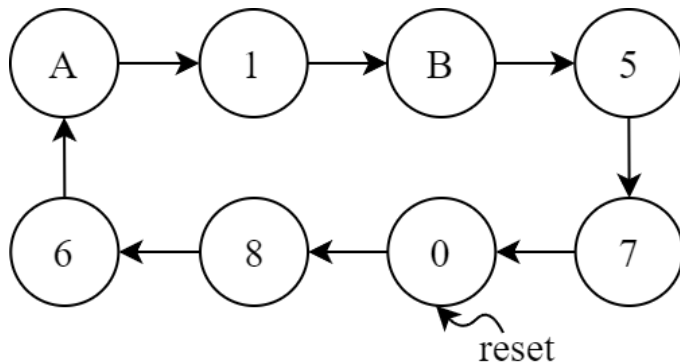- State table: Assume 01057086 $\rightarrow$ A1B57086



Current status (t)					Next status ($t + 1$)				
ID	$W(t)$	$X(t)$	$Y(t)$	$Z(t)$	$W(t + 1)$	$X(t + 1)$	$Y(t + 1)$	$Z(t + 1)$	ID
0	0	0	0	0	1	0	0	0	8
1	0	0	0	1	1	0	1	1	B
	0	0	1	0	X	X	X	X	
	0	0	1	1	X	X	X	X	
	0	1	0	0	X	X	X	X	
5	0	1	0	1	0	1	1	1	7
6	0	1	1	0	1	0	1	0	A
7	0	1	1	1	0	0	0	0	0
8	1	0	0	0	0	1	1	0	6
	1	0	0	1	X	X	X	X	
A	1	0	1	0	0	0	0	1	1
B	1	0	1	1	0	1	0	1	5
	1	1	0	0	X	X	X	X	
	1	1	0	1	X	X	X	X	
	1	1	1	0	X	X	X	X	
	1	1	1	1	X	X	X	X	

LAB 1 – Display Student ID (4/5)

- Testbench

```
module test_student_id;

    logic clk, reset;
    logic [3:0] id;

    student_id id1(
        .clk(clk),
        .reset(reset),
        .id(id)
    );


    always #5 clk = ~clk;

    initial begin
        clk = 0; reset = 1;
        #10 reset = 0;
        #500 $stop;
    end

endmodule
```

LAB 1 – Display Student ID (5/5)

- Waveform: Assume 01057086 → A1B57086

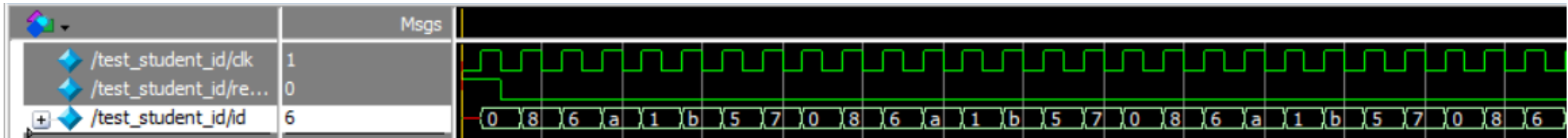

- When downloading to the DE0 board, the clock must pass through a frequency divider before use.
 - Use freq_div_23 designed in Lab 9
- The output student_id should be connected to the seven-segment display.

```

freq_div_23 fre_23(
    .clk      (CLK),
    .reset    (~BTN[0]),
    .clk_out   (clk_out)
);

student_id id1(
    .clk(clk_out),
    .reset(~BTN[0]),
    .student_id(id)
);

seven_segment s0(
    .in  (id),
    .out (HEX0)
);
    
```

LAB 2 – Display Birthday (1/3)

- Design a Finite State Machine (FSM) that outputs digits of a birthday in the format of YYMMDD one by one.
 - For example, if the birthday is June 17, 2010, it will be formatted as 0100617.
- When a repeated digit is encountered, the second occurrence of the repeated digit is replaced with 'F', the third one is replaced with 'E', and so on.
 - For example, 0990617 becomes 09FE617. The first occurrence of a repeated digit remains unchanged.

LAB 2 – Display Birthday (2/3)

- Rules for modifying repeated digits in the birthday:
 - The first occurrence of a repeated digit remains unchanged, while all previous occurrences are replaced sequentially with the letters F, E, D, C, B, A.
 - For example, 0981217 becomes 09811F7.
 - When there are multiple sets of repeated digits in the birthdate, replace them in order of appearance using letters from F to A.
 - For example, 0990617 becomes 09FE617.
- If you are unsure how to convert your birthday, please ask the TA for help.

LAB 2 – Display Birthday (3/3)

- Signal settings
 - Input: clk and reset
 - Output: birthday [3:0]
- State diagram: Assume 0990617 → 09FE617
- When downloading to the DE0 board, the clock must pass through a frequency divider before use.
 - Use freq_div_23 designed in Lab 9
- The output should be connected to the seven-segment display.

