



Lab 2

Basic Logic Gate Implementation

Part 2

Prof. Chih-Cheng Tseng (曾志成)

cctseng@mail.ntou.edu.tw

Contents of this slide are provided by NTOU VLSI Lab601

Objectives


- Understand following components
 - Transistor-Transistor Logic (TTL) ICs 7400, 7404, 7408, 7432
- Implement **logic circuits** to verify the corresponding **truth tables**

TTL 7400 (NAND)


Figure Sources:

- <https://www.igelectronics.com/products/g69b66b32e/1726810000000161177>
- <https://www.build-electronic-circuits.com/7400-series-integrated-circuits/74hc00-74ls00/>

Physical Packaging

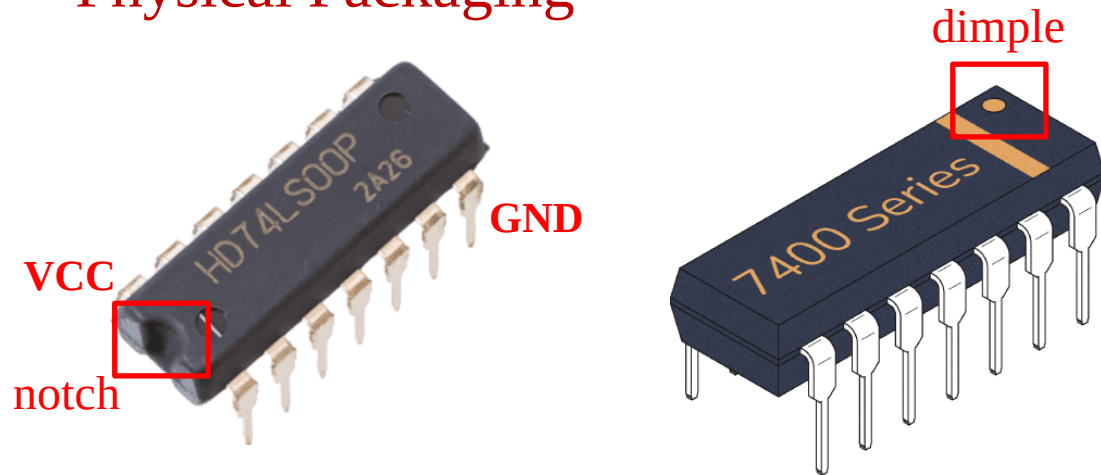

Internal Structure

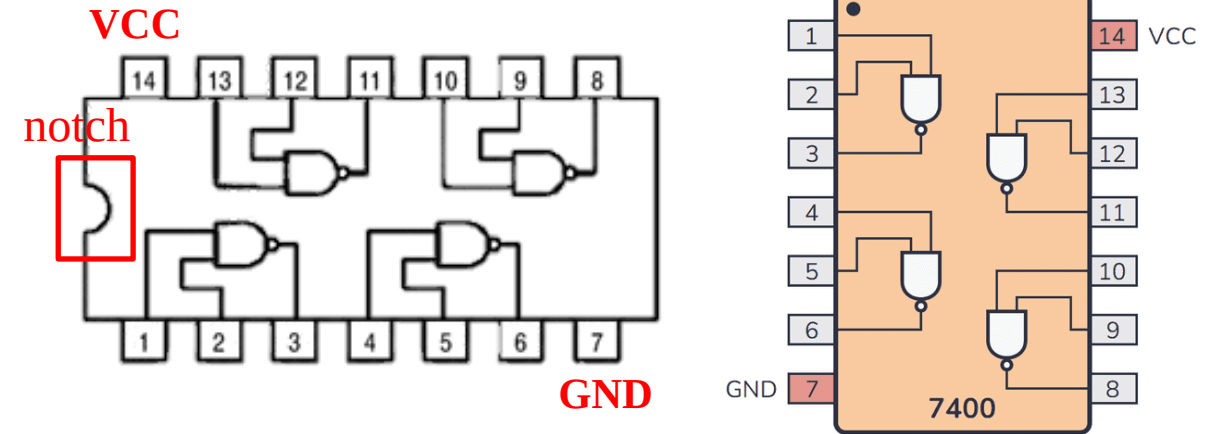

Graphic Symbol



Truth Table


Input A	Input B	Output OUT
0	0	1
0	1	1
1	0	1
1	1	0

TTL 7404 (NOT)


Figure Source:

1. https://pt.wikipedia.org/wiki/TTL_7404


Physical Packaging

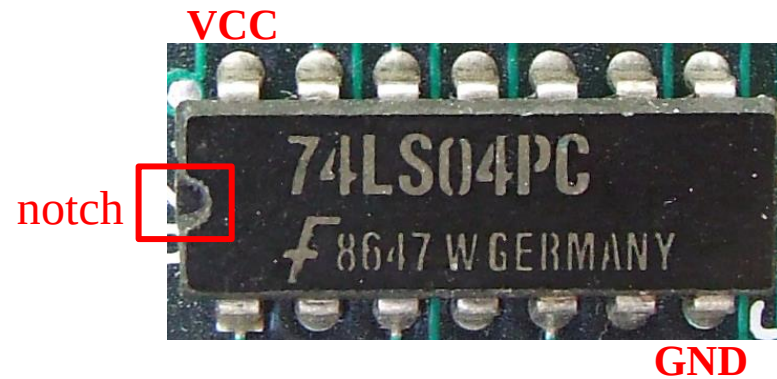

Internal Structure

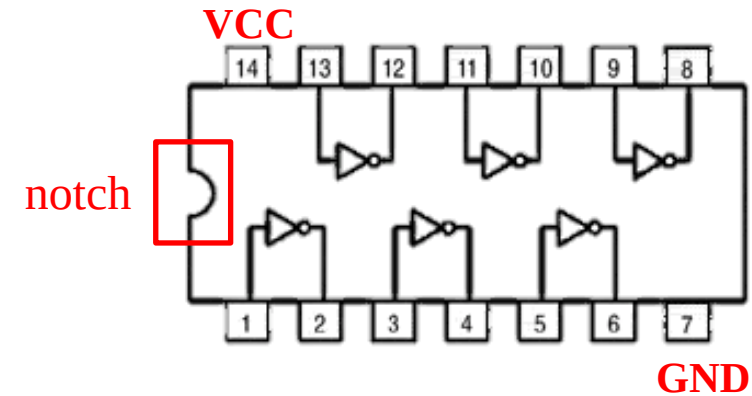

Graphic Symbol

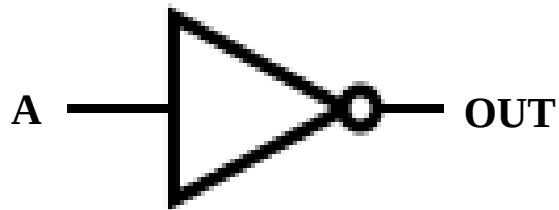

Truth Table

Input A	Output OUT
0	1
1	0


TTL 7408 (AND)

Figure Source:
1. https://pt.wikipedia.org/wiki/TTL_7408


Physical Packaging



Internal Structure

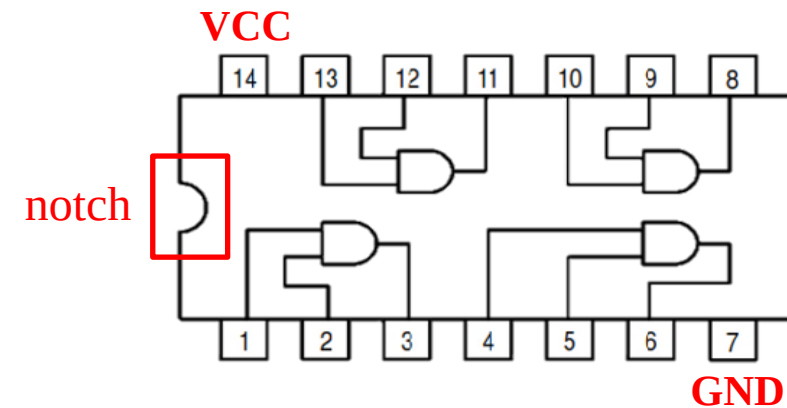

Graphic Symbol

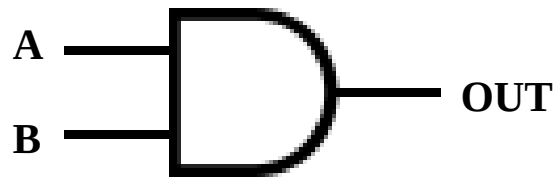

Truth Table

Input A	Input B	Output OUT
0	0	0
0	1	0
1	0	0
1	1	1

TTL 7432 (OR)


Figure Source:

<https://docs.cirkitdesigner.com/component/e39cedd2-1d38-4573-829f-9f133c89a3b8/7432-or-gate-ic>


Physical Packaging



Internal Structure

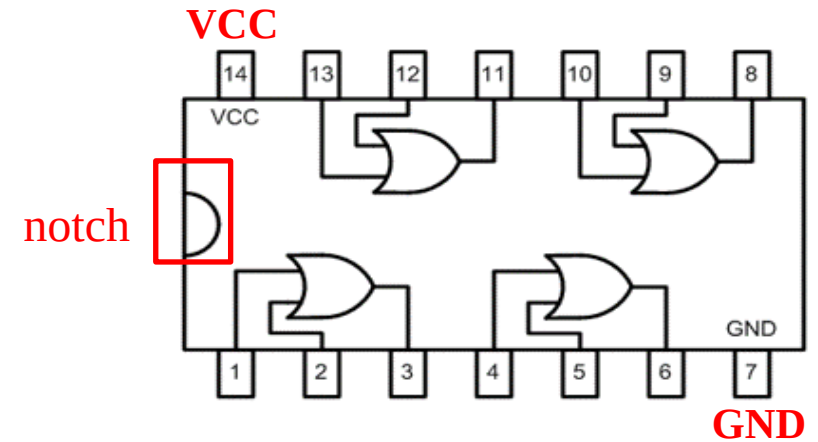

Graphic Symbol

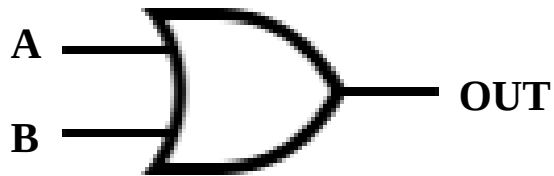


Truth Table

Input A	Input B	Output OUT
0	0	0
0	1	1
1	0	1
1	1	1

Number/Alphabet vs Logic State



- 0 → Logic LOW (Ground)
- 1 → Logic HIGH (5V)
- x or X → Undefined
- z or Z → High Impedence or Floating
- When an input pin of a TTL IC is floating, it is typically interpreted as a logic HIGH (1).

Voltage Logic Levels

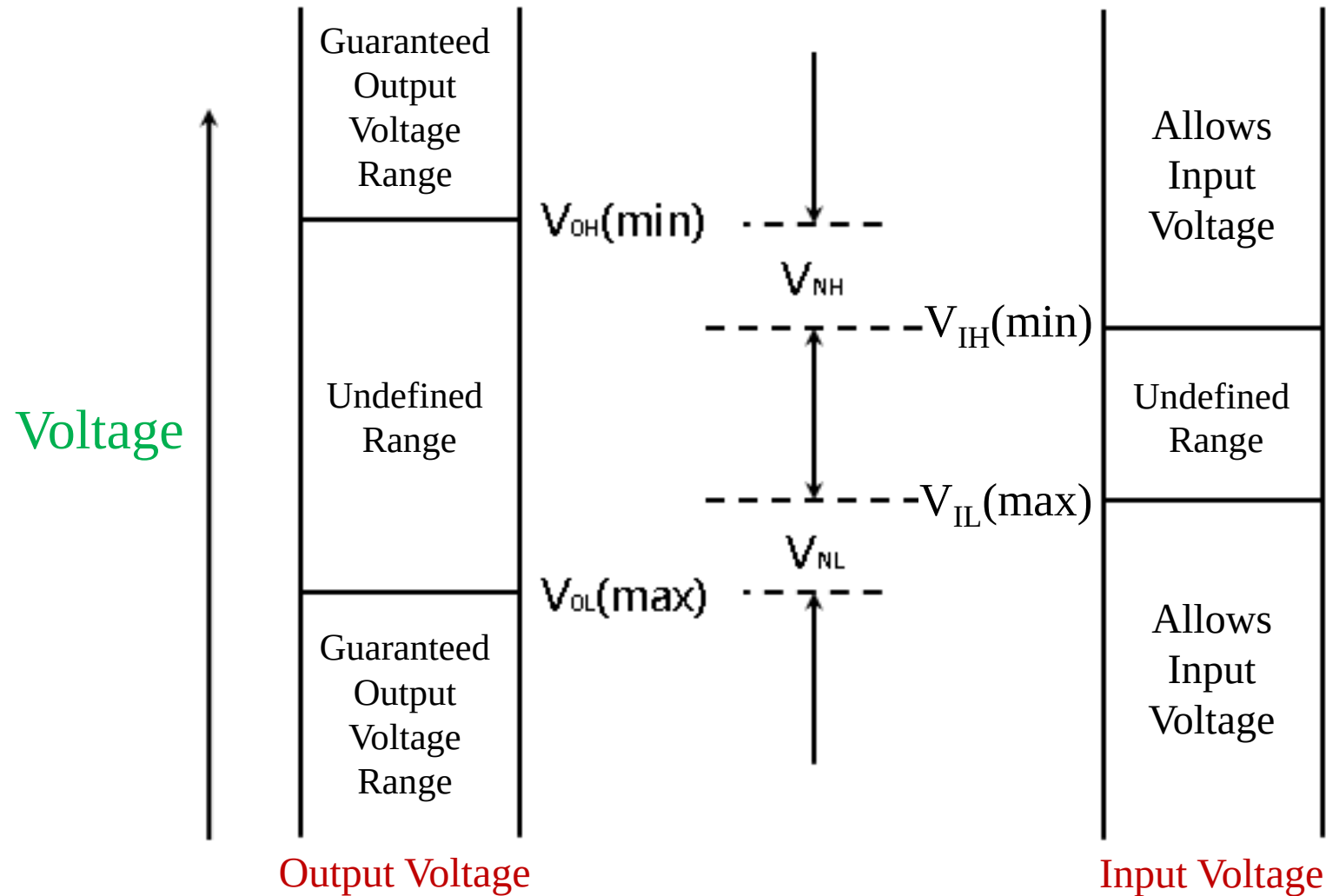

Example of Voltage Logic Levels --- Standard TTL

TTL Type	IC Number	$V_{OH}(\text{min})$	$V_{IH}(\text{min})$	$V_{OL}(\text{max})$	$V_{IL}(\text{max})$	Propagation Delay	Power Consumption
Standard	74xx	2.4V	2.0V	0.4V	0.8V	9 ns	10 mW

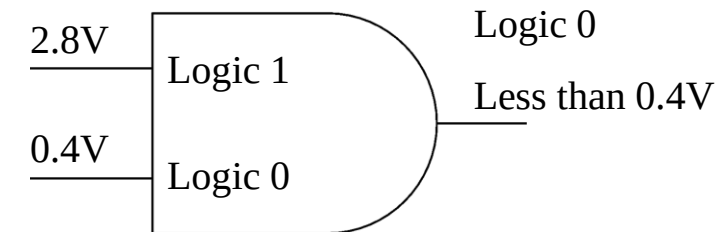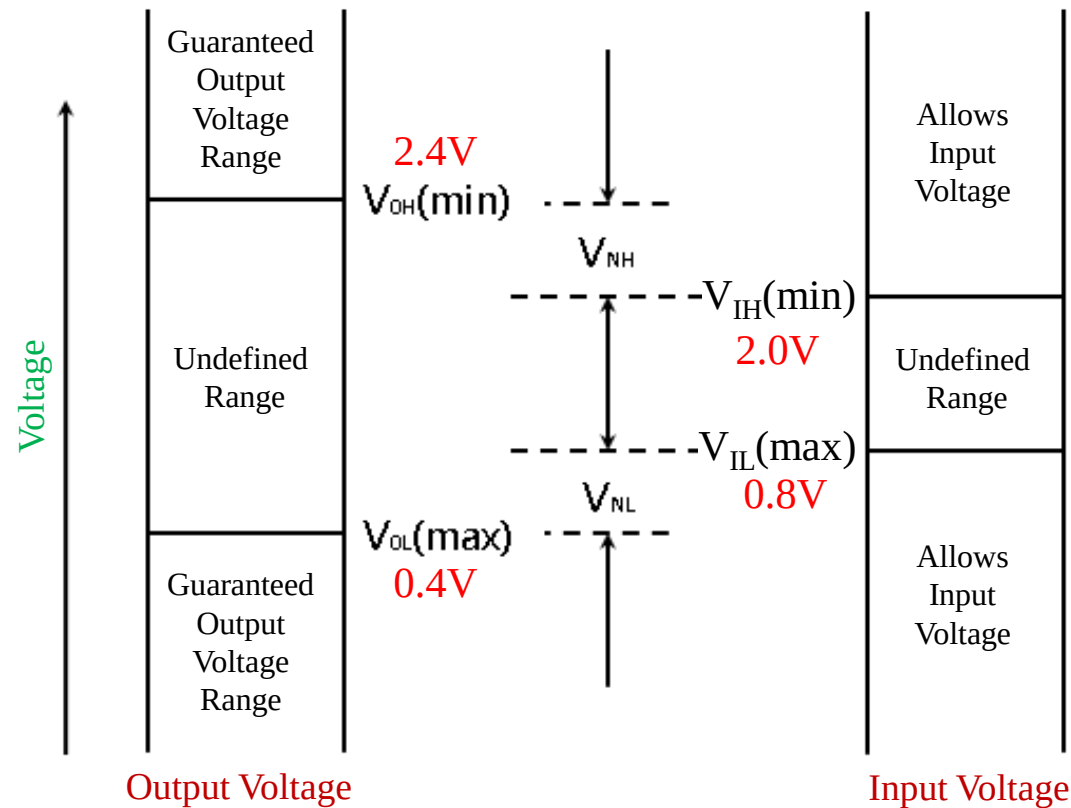


Comparison Table

TTL Type	IC Number	$V_{OH}(\text{min})$	$V_{IH}(\text{min})$	$V_{OL}(\text{max})$	$V_{IL}(\text{max})$	Propagation Delay	Power Consumption
Standard	74xx	2.4V	2.0V	0.4V	0.8V	9 ns	10 mW
Low Power	74Lxx	2.4V	2.0V	0.3V	0.8V	33 ns	1 mW
High-Speed	74Hxx	2.4V	2.0V	0.4V	0.8V	6 ns	23 mW
Schottky (high-speed with the same power consumption)	74Sxx	2.4V	2.0V	0.5V	0.8V	3 ns	23 mW
Low Power Schottky	74LSxx	2.4V	2.0V	0.5V	0.8V	9.5 ns	2 mW

LAB 2-1

- Implement the circuit shown in the diagram.
- Two truth tables must be provided (Measured Voltage and Logic).
- The output must be connected to an LED.
- Photos must be taken for each scenario.

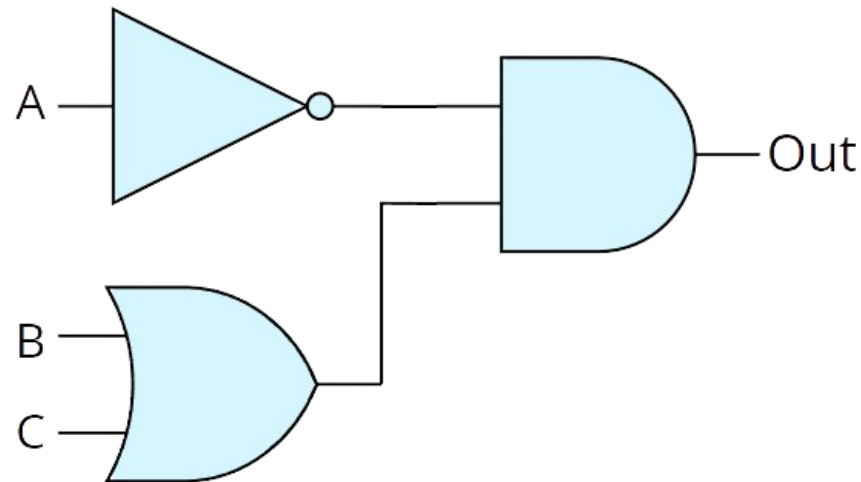

LAB 2-2

- Implement the circuit shown in the diagram.
- Two truth tables must be provided (Measured Voltage and Logic).
- The output must be connected to an LED.
- Photos must be taken for each scenario.

