



# Lab 5

## Basic Logic Gate Implementation

### Part 5

**Prof. Chih-Cheng Tseng (曾志成)**

[cctseng@mail.ntou.edu.tw](mailto:cctseng@mail.ntou.edu.tw)

Contents of this slide are provided by NTOU VLSI Lab601


# Objectives

---

- Learn the operation principle of adders.
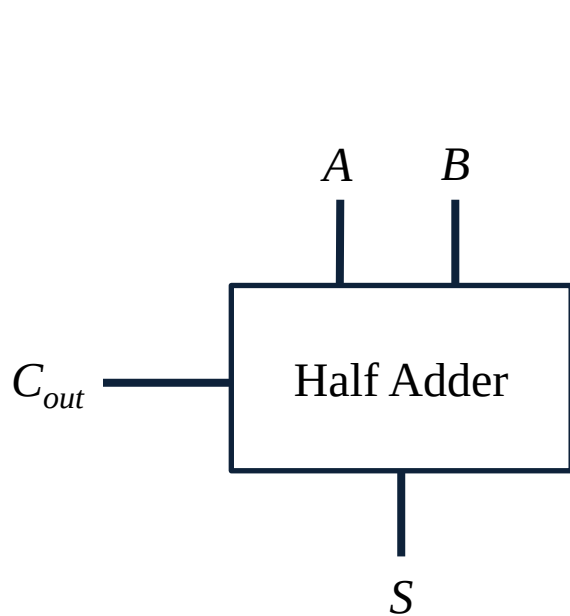
# 1-bit Half Adder

- The half adder only considers the two numbers being added and does not account for carry from the previous stage.



**S**

|          |          |   |   |
|----------|----------|---|---|
|          | <b>B</b> | 0 | 1 |
| <b>A</b> | 0        | 0 | 1 |
|          | 1        | 1 | 0 |


**C<sub>out</sub>**

|          |          |   |   |
|----------|----------|---|---|
|          | <b>B</b> | 0 | 1 |
| <b>A</b> | 0        | 0 | 0 |
|          | 1        | 0 | 1 |

| Truth Table |   |                  |   |
|-------------|---|------------------|---|
| Input       |   | Output           |   |
| A           | B | C <sub>out</sub> | S |
| 0           | 0 | 0                | 0 |
| 0           | 1 | 0                | 1 |
| 1           | 0 | 0                | 1 |
| 1           | 1 | 1                | 0 |
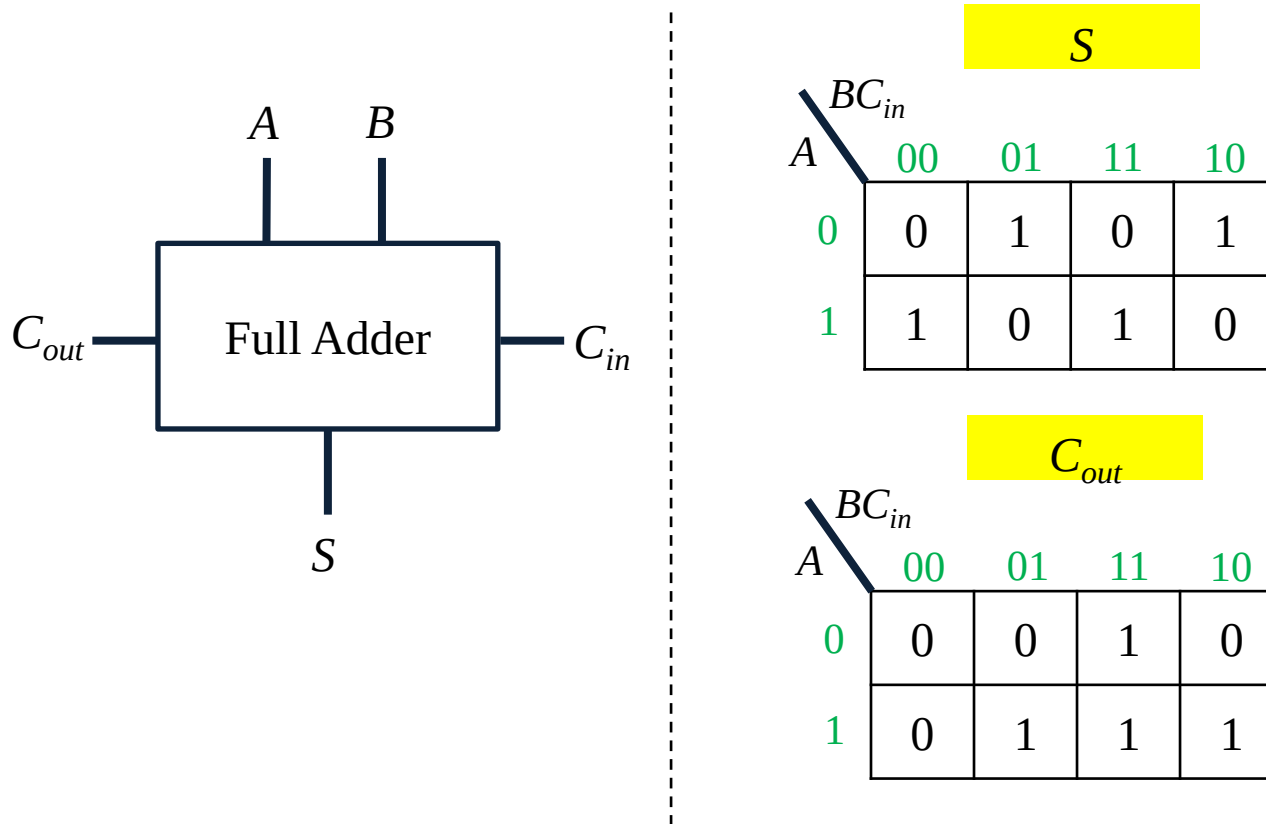
# 1-bit Full Adder

- The full adder accounts for carry from the previous stage.



| Truth Table |     |          |           |     |
|-------------|-----|----------|-----------|-----|
| Input       |     |          | Output    |     |
| $A$         | $B$ | $C_{in}$ | $C_{out}$ | $S$ |
| 0           | 0   | 0        | 0         | 0   |
| 0           | 0   | 1        | 0         | 1   |
| 0           | 1   | 0        | 0         | 1   |
| 0           | 1   | 1        | 1         | 0   |
| 1           | 0   | 0        | 0         | 1   |
| 1           | 0   | 1        | 1         | 0   |
| 1           | 1   | 0        | 1         | 0   |
| 1           | 1   | 1        | 1         | 1   |

# LAB 5-1


- Implement the half adder circuit.
  1. Draw the truth table.
  2. Draw the Karnaugh map (K-map).
  3. Simplify the Boolean algebra to its simplest form.
  4. Draw the logic circuit diagram.
  5. Implement this logic circuit on a breadboard.
  6. Take pictures of each experiment result.
  
- Please add LEDs to the output.

## LAB 5-2

- Implement the full adder circuit.
  1. Draw the truth table.
  2. Draw the Karnaugh map (K-map).
  3. Simplify the Boolean algebra to its simplest form.
  4. Draw the logic circuit diagram.
  5. Implement this logic circuit on a breadboard.
  6. Take pictures of each experiment result.
  
- Please add LEDs to the output.
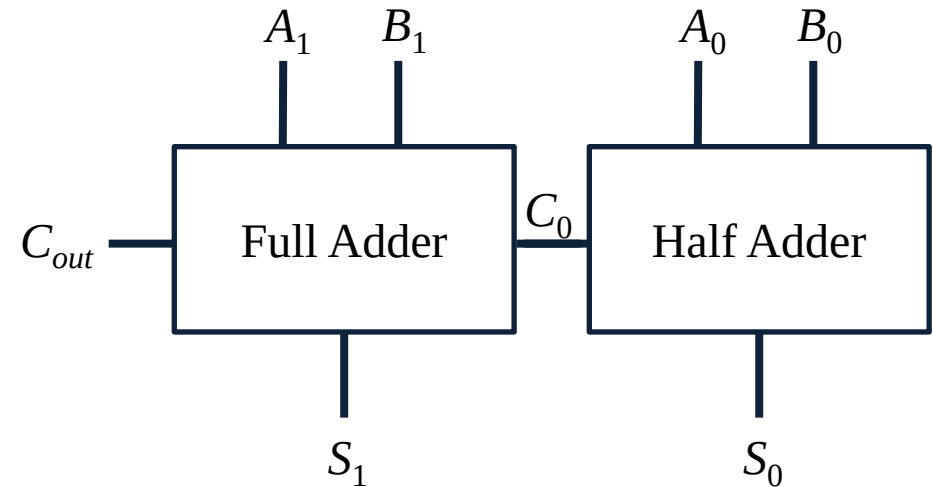
## LAB 5-3

- Using 1-bit half adder and 1-bit full adder to design a 2-bit adder.
  1. Draw the truth table.
  2. Draw the Karnaugh map (K-map).
  3. Simplify the Boolean algebra to its simplest form.
  4. Draw the logic circuit diagram.
  5. Implement this logic circuit on a breadboard.
  6. Take pictures of each experiment result.
- Please add LEDs to the output.



## Bonus

- Design a 2-bit subtractor by using the 1-bit full adder. (Tips:  $A - B = A + (2\text{'s complement of } B)$ .)
  1. Draw the truth table.
  2. Simplify the Boolean algebra to its simplest form.
  3. Draw the logic circuit diagram.
  4. Implement this logic circuit on a breadboard.
- Please add LEDs to the output.