



本教學投影片係屬教科書著作之延伸，亦受著作權法之保護。

請依出版社授權使用規範利用本教學資源，非經授權許可不得以影印、拷貝、列印等方法進行重製，亦不得改作、公開展示著作內容，亦請勿對第三人公開傳輸、散布。



Chapter 6

Registers and Counters

Prof. Chih-Cheng Tseng (曾志成)

cctseng@mail.ntou.edu.tw

Chapter Objectives

- Understand the use, functionality, and modes of operation of registers, shift registers (移位暫存器), and universal shift registers.
- Know how to properly create the effect of a gated clock (閘控時脈).
- Understand the structure and functionality of a serial adder circuit.
- Understand the behavior of a (a) ripple counter, (b) synchronous counter, (c) ring counter, and (d) Johnson counter.
連波計數器 同步計數器 環形計數器 詹森計數器
- Be able to write structural and behavioral HDL models of registers, shift registers, universal shift registers, and counters.

6.1 Registers (1/3)

- Clocked sequential circuits (CSC) (時控序向電路)
 - A group of flip-flops and combinational gates connected to form a feedback path.

Flip-flops + Combinational gates
 (essential) (optional)
- Based on the functions, CSCs are classified 利用功能的不同將CSC分類.....
 - Register (暫存器)
 - Flip-flops hold the binary information. / 將資料在暫存器間轉移
 - Combinational gates determine how the information is transferred into the register.
 - Counter (計數器)
 - A special register that goes through a predetermined sequence of binary states.
 - The combinational gates are connected in such a way as to produce the prescribed sequence of states.

6.1 Registers (2/3)

* D 型 正反器 → 透 通 形 正 反 器

輸入直接反應給輸出

- An n -bit register
 - n flip-flops capable of storing n bits of binary information
- Consider the 4-bit register in Figure 6.1,
 - If the contents of the register must be left unchanged,
 - The inputs must be held constant.
 - This would result in the data bus (匯流排) driving the register being unavailable for other traffic.
 - The clock must be inhibited from the circuit by inserting some control gates into the clock path.
 - This would result in uneven propagation delays between the global clock and the inputs of flip-flops.
 - Solution: Gated clock 閘控時脈 (沒有真正控制 clock, 而是利用 D 型正反器設計輸入來達成控制 clock 的效果)
 - Control the operation of the register with the D inputs, rather than the clock in the C inputs. 不能直接控制 clock, 会造成時間差。

 


FIGURE 6.1
Four-bit register

6.1 Registers (3/3)

4-bit register with parallel load

- The transfer of new information into a register is referred to as *loading* or *updating*.
- If all the bits of the register are loaded simultaneously with a common clock pulse, the loading is regarded as *parallel*.

許多人(輸入源)共用一條線
↑

*匯流排 Bus


 
 


FIGURE 6.2
Four-bit register with parallel load

 

6.2 Shift Registers (1/12) 移位暫存器

- Shift register
 - a register capable of shifting its binary information in one or both directions
- Simplest shift register

 


FIGURE 6.3
Four-bit shift register

6.2 Shift Registers (2/12)

- **Practice Exercise 6.1 Objective:** Draw the logic diagram of a circuit that suspends the clock action of a D flip-flop without gating its clock. Describe the behavior of the circuit.

Answer:

 


FIGURE PE6.1

If $Data_gate$ is 0, $Data$ is transferred to Q with each active edge of $clock$. If $Data_gate$ is 1, the value of Q is recirculated through the mux-flip-flop path, with the effect that $clock$ appears to be suspended.

6.2 Shift Registers (3/12)

- Serial transfer 串列傳輸
 - Information is transferred one bit at a time by shifting the bits out of the source register into the destination register
- Parallel transfer
 - All the bits of the register are transferred at the same time

6.2 Shift Registers (4/12)

Serial Transfer

 


FIGURE 6.4
Serial transfer from register A to register B

6.2 Shift Registers (5/12)

Serial Addition

- Serial addition using D flip-flops
 - Assume $Q = 0$ initially.

$$A \leq A + B$$

$$\begin{array}{r}
 111 \\
 0101 \\
 + 0011 \\
 \hline
 1000
 \end{array}$$

 


FIGURE 6.5
Serial adder

6.2 Shift Registers (6/12)

Serial Addition

- Serial adder using JK flip-flops

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

- Try to redesign with
 - D F/F
 - T F/F

Table 6.2
State Table for Serial Adder

Present State Q	Inputs x y		Next State Q	Output S	Flip-Flop Inputs	
					J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

6.2 Shift Registers (7/12)

Serial Addition

- Circuit diagram

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

 


FIGURE 6.6
Second form of serial adder

6.2 Shift Registers (8/12)

Universal Shift Register

- Unidirectional shift register
- Bidirectional shift register
- Universal shift register: 萬用移位暫存器
 - has both direction shifts & parallel load/out capabilities

6.2 Shift Registers (9/12)

Universal Shift Register

- Capability of a universal shift register:
 - 1. A *clear* control to clear the register to 0.
 - 2. A *clock* input to synchronize the operations.
 - 3. A *shift-right* control to enable the shift right operation and the *serial input* and *output* lines associated w/ (with) the shift right.
 - 4. A *shift-left* control to enable the shift left operation and the *serial input* and *output* lines associated w/ (with) the shift left.
 - 5. A *parallel-load* control to enable a parallel transfer and the n *parallel input* lines associated w/ the parallel transfer.
 - 6. n *parallel output* lines.
 - 7. A control state that leaves the information in the register unchanged in the presence of the clock.

左移、右移
串列/序列 進出
重設 Clear

6.2 Shift Registers (10/12)

Universal Shift Register

- Example: 4-bit universal shift register

 


Table 6.3
Function Table for the Register of Fig. 6.7

Mode Control		Register Operation
s_1	s_0	
0	0	No change
0	1	Shift right 右移
1	0	Shift left 左移
1	1	Parallel load 並列輸入

FIGURE 6.7
Four-bit universal shift register

6.2 Shift Registers (11/12)

Universal Shift Register

Mode Control		
s_1	s_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


 


FIGURE 6.7
Four-bit universal shift register

 

6.3 Ripple Counters (1/7)

連波計數器

- Counter

- A register that goes through a prescribed sequence of states.
- Upon the application of input pulses, the sequence of states may follow the binary number sequence (→ Binary counter) or any other sequence of states
 - The input pulses may be clock pulses or originate from some external source

- Categories of counters

(非同步計數器)

1. Ripple counters (連波計數器)

The flip-flop output transition serves as a source for triggering other flip-flops
 ⇒ no common clock pulse (not synchronous)

2. Synchronous counters (同步計數器)

The CLK inputs of all flip-flops receive a common clock

6.3 Ripple Counters (2/7)

Binary Ripple Counter

- Example: 4-bit binary ripple counter
 - Binary count sequence: 4-bit

Table 6.4
Binary Count Sequence

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

6.3 Ripple Counters (3/7)

Binary Ripple Counter

功能都一樣!
(負緣觸發)

 



FIGURE 6.8
Four-bit binary ripple counter

典型的Ripple Counter
(注意clk! DFF們並沒有共享clk)
(Not a Synchronous Counter!)

6.3 Ripple Counters (4/7)

Binary Ripple Counter

- Timing diagram (with T flip-flops)

 

<key 速度会变慢!>

6.3 Ripple Counters (5/7)

BCD Ripple Counter


 


FIGURE 6.9
State diagram of a decimal BCD counter

6.3 Ripple Counters (6/7)

BCD Ripple Counter BCD 漣波計數器 (BCD 非同步計數器)

FIGURE 6.10
BCD ripple counter

 

● Case 1: 0111 (left figure)


 
 


FIGURE 6.10
BCD ripple counter

● Case 2: 1001 (right figure)

 

6.3 Ripple Counters (7/7)

BCD Ripple Counter

- Three-decade BCD counter 一个BCD计数器 → 数一个十进制

 


FIGURE 6.11

Block diagram of a three-decade decimal BCD counter

數三个十进制

6.4 Synchronous Counters (1/8)

- Synchronous counter 同步計數器
 - A common clock triggers all flip-flops simultaneously. → 所有正反器共享一個 CLK.
- Design procedure
 - Apply the same procedure of synchronous sequential ckts (circuits).
 - Synchronous counter is simpler than general synchronous sequential ckts.
設計同步計數器 將會比設計序項邏輯來的簡單！

6.4 Synchronous Counters (2/8)

Binary Counter

4 个 DFF $\Rightarrow 2^4 = 16 (0 \sim 15)$


 


FIGURE 6.12 Four-bit synchronous binary counter

JK 正反器的 J、K 都接一起 $\Rightarrow$ 当成 T 型正反器!

Count Enable 为 0, 不计数!!

 

$\hookrightarrow$ 假设不把他当计数器, 每个 DFF 都看成一个新的 CLK $\Rightarrow$ 除频器, A_0 的频率就是原始 CLK 频率的 $\frac{1}{2}$!

只能同時有一個
是 1 !

[illegible]

6.4 Synchronous Counters (4/8)

BCD Counters → 只有 0~9 而已!

Table 6.5
State Table for BCD Counter.

Present State					Next State					Output	Flip-Flop Inputs			
Q ₈	Q ₄	Q ₂	Q ₁	DEC	Q ₈	Q ₄	Q ₂	Q ₁	DEC	y	T _{Q8}	T _{Q4}	T _{Q2}	T _{Q1}
0	0	0	0	0	0	0	0	1	1	0	0	0	0	1
0	0	0	1	1	0	0	1	0	2	0	0	0	1	1
0	0	1	0	2	0	0	1	1	3	0	0	0	0	1
0	0	1	1	3	0	1	0	0	4	0	0	1	1	1
0	1	0	0	4	0	1	0	1	5	0	0	0	0	1
0	1	0	1	5	0	1	1	0	6	0	0	0	1	1
0	1	1	0	6	0	1	1	1	7	0	0	0	0	1
0	1	1	1	7	1	0	0	0	8	0	1	1	1	1
1	0	0	0	8	1	0	0	1	9	0	0	0	0	1
1	0	0	1	9	0	0	0	0	0	1	1	0	0	1

- Simplified functions:

$$T_{Q1} = 1$$

$$T_{Q2} = Q_8'Q_1$$

$$T_{Q4} = Q_2Q_1$$

$$T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$

$$y = Q_8Q_1$$

6.4 Synchronous Counters (5/8)

Binary Counter with Parallel Load

Table 6.6

Function Table for the Counter of Fig. 6.14

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

 


FIGURE 6.14

Four-bit binary counter with parallel load

6.4 Synchronous Counters (6/8)

Binary Counter with Parallel Load

Table 6.6
Function Table for the Counter of Fig. 6.14

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

 


FIGURE 6.14
Four-bit binary counter with parallel load

6.4 Synchronous Counters (7/8)

Binary Counter with Parallel Load

- Generate any count sequence
 - E.g.: BCD counter $\Leftarrow$ Counter w/ parallel load

 


FIGURE 6.15

Two ways to achieve a BCD counter using a counter with parallel load

6.4 Synchronous Counters (8/8)

Binary Counter with Parallel Load

- **Practice Exercise 6.3** How do a ripple counter and a synchronous counter differ in their behavior?

Answer: All of the flip-flops in a synchronous counter are synchronized by receiving a common clock pulse; only the first stage of a ripple counter receives a clock pulse. The stages of a synchronous counter are updated simultaneously by a common clock; the stages of a ripple counter are updated one at a time. A synchronous counter operates faster than a ripple counter.

6.5 Other Counters (1/12)

- Counters:
 - can be designed to generate any desired sequence of states
- Divide-by- N counter (modulo- N counter)
 - a counter that goes through a repeated sequence of N states
 - The sequence may follow the binary count or may be any other arbitrary sequence

6.5 Other Counters (2/12)

Counter with Unused States

- n flip-flops $\Rightarrow 2^n$ binary states → 增加一个正反器, 多一个 2^n 次方的计数
- Unused states
 - states that are not used in specifying the FSM
 - may be treated as don't-care conditions or may be assigned specific next states
- Self-correcting counter
 - Ensure that when a ckt enter one of its unused states, it eventually goes into one of the valid states after one or more clock pulses so it can resume normal operation.
 $\Rightarrow$ Analyze the ckt to determine the next state from an unused state after it is designed


6.5 Other Counters (3/12)

Counter with Unused States

● An example

Table 6.7
State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
0	1	1	1	0	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	1	1	0	1

 

(b) State transition diagram

Two unused states: 011 & 111

BC	00	01	11	10
A	0	0	X=1	1
1	X	X	X=1	X

$$J_A = B$$

BC	00	01	11	10
A	0	1	X=1	X
1	0	1	X=1	X

$$J_B = C$$

BC	00	01	11	10
A	0	1	X=0	0
1	1	X	X=0	0

$$J_C = B'$$

BC	00	01	11	10
A	0	X	X=1	X
1	0	1	X=1	X

$$K_A = B$$

BC	00	01	11	10
A	0	X	X=1	1
1	X	X	X=1	1

$$K_B = 1$$

BC	00	01	11	10
A	0	X	1	X=1
1	X	1	X=1	X

$$K_C = 1$$

6.5 Other Counters (4/12)

Counter with Unused States

- The logic diagram & state diagram of the circuit
- The simplified flip-flop input equations:

$$J_A = B, \quad K_A = B$$

$$J_B = C, \quad K_B = 1$$

$$J_C = B', \quad K_C = 1$$


 


FIGURE 6.16
Counter with unused states

 

6.5 Other Counters (5/12)

Ring Counter 環形計數器


- A circular shift register with only one flip-flop being set at any particular time, all others are cleared, i.e., initial value = 1 0 0 ... 0
- The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals.

6.5 Other Counters (6/12)

Ring Counter

- A 4-bit ring counter

A_2	A_2	A_1	A_0
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
1	0	0	0

 

(a) Ring-counter (initial value = 1000)

FIGURE 6.17
Generation of timing signals

6.5 Other Counters (7/11)

Ring Counter

- Approaches for the generation of 2^n timing signals to control the sequence of operations in a digital system
 - a shift register w/ 2^n flip-flops
 - an n -bit binary counter together w/ an n -to- 2^n -line decoder

 
 
 


FIGURE 6.17
Generation of timing signals

6.5 Other Counters (8/11)

Johnson Counter

- Ring counter vs. Switch-tail (切換-尾端) ring counter
 - Ring counter
 - A k -bit ring counter circulates a single bit among the flip-flops to provide k distinguishable states.
 - Switch-tail ring counter
 - A circular shift register w/ the complement output of the last flip-flop connected to the input of the first flip-flop
 - A k -bit switch-tail ring counter will go through a sequence of $2k$ distinguishable states. (initial value = 0 0 ... 0)


Ring Counter: K 個 → 數 K 個狀態、初值確保一個為 1, 其他都是 0。

Switch-tail Counter (Johnson Counter): K 個 → 數 $2K$ 個狀態、初值確保全部都是 0!

6.5 Other Counters (10/12)

Johnson Counter

- An example: Switch-tail ring counter

 

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

→ 要有 8 个 AND Gates,
每个 Gates 都是兩輸入, 來確保結果!

(b) Count sequence and required decoding

FIGURE 6.18
Construction of a Johnson counter

6.5 Other Counters (11/12)

Johnson Counter

- Johnson counter
 - a k -bit switch-tail ring counter + $2k$ decoding gates
 - provide outputs for $2k$ timing signals
 - E.g.: 4-bit Johnson counter

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

- The decoding follows a regular pattern:
 - 2 inputs per decoding gate

6.5 Other Counters (11/11)

Johnson Counter

- Disadvantages of the switch-tail ring counter
 - If it finds itself in an unused state, it will persist to circulate in the invalid states and never find its way to a valid state.
 - One correcting procedure is $D_C = (A + C)B$
- Summary
 - Johnson counters can be constructed for any # of timing sequences:
 - # of flip-flops = 1/2 (the # of timing signals)
 - # of decoding gates = # of timing signals
 - 2-input per decoding AND gate

Question! How to design a k-bit Johnson counter that generates $(2k-1)$ timing signals?

6.6 HDL for Registers and Counters (1/12)

Shift Register

- Statement: $A_par \leq \{MSB_in, A_par[3:1]\}$
 - specifies a concatenation of serial data input for a right shift operation (*MSB_in*) with bits *A_par[3 : 1]* of the output data bus.

6.6 HDL for Registers and Counters (2/12)

Shift Register

- HDL Example 6.1 (Universal Shift Register-Behavioral Model)

Verilog

```
// Behavioral description of a 4-bit universal shift register
// Fig. 6.7 and Table 6.3
module Shift_Register_4_beh (                                // V2001, 2005 syntax
    output reg [3: 0] A_par,                                // Register output
    input [3: 0] I_par,                                     // Parallel input
    input s1, s0,                                           // Select inputs
    MSB_in, LSB_in,                                         // Serial inputs
    CLK, Clear_b                                           // Clock and active-low clear
);
always @ (posedge CLK, negedge Clear_b)                    // V2001, 2005 syntax
    if (Clear_b == 0) A_par <= 4'b000;
    else
        case ({s1, s0})
            2'b00: A_par <= A_par;                          // No change
            2'b01: A_par <= {MSB_in, A_par[3: 1]};          // Shift right
            2'b10: A_par <= {A_par[2: 0], LSB_in};          // Shift left
            2'b11: A_par <= I_par;                          // Parallel load of input
        endcase
    endmodule
```

6.6 HDL for Registers and Counters (3/12)

Shift Register

- Variables of type **reg.** retain their value until they are assigned a new value by an assignment statement. Consider the following alternative **case** statement for the shift register model:

```

case ({s1, s0})
    // 2'b00: A_par <= A_par;           // No change
    2'b01: A_par <= {MSB_in, A_par [3: 1]}; // Shift right
    2'b10: A_par <= {A_par [2: 0], LSB_in}; // Shift left
    2'b11: A_par <= I_par;             // Parallel load of input
endcase

```

6.6 HDL for Registers and Counters (4/12)

Shift Register

- HDL Example 6.2 (Universal Shift Register-Structural Model)

```
// Structural description of a 4-bit universal shift register (see Fig. 6.7)
module Shift_Register_4_str (                                // V2001, 2005
    output [3: 0]  A_par,                                     // Parallel output
    input [3: 0]   I_par,                                     // Parallel input
    input          s1, s0,                                   // Mode select
    input          MSB_in, LSB_in, CLK, Clear_b             // Serial inputs, clock, clear
);

// bus for mode control
wire  [1:0]  select = {s1, s0};

// Instantiate the four stages
stage ST0 (A_par[0], A_par[1], LSB_in, I_par[0], A_par[0], select, CLK, Clear_b);
stage ST1 (A_par[1], A_par[2], A_par[0], I_par[1], A_par[1], select, CLK, Clear_b);
stage ST2 (A_par[2], A_par[3], A_par[1], I_par[2], A_par[2], select, CLK, Clear_b);
stage ST3 (A_par[3], MSB_in, A_par[2], I_par[3], A_par[3], select, CLK, Clear_b);
endmodule
```

6.6 HDL for Registers and Counters (5/12)

Shift Register

- HDL Example 6.2 (Universal Shift Register-Structural Model)

```
// One stage of shift register
module stage (i0, i1, i2, i3, Q, select, CLK, Clr_b);
  input      i0,           // circulation bit selection
              i1,           // data from left neighbor or serial input for shift-right
              i2,           // data from right neighbor or serial input for shift-left
              i3;           // data from parallel input

  output     Q;

  input [1: 0] select;      // stage mode control bus
  input      CLK, Clr_b;    // Clock, Clear for flip-flops
  wire       mux_out;

  // instantiate mux and flip-flop
  wire Clr = ~Clr_b        // Flip-flop has active-high clear signal
                          // but circuit has active-low clear action

  Mux_4x1     M0            (mux_out, i0, i1, i2, i3, select);
  D_flip_flop M1            (Q, mux_out, CLK, Clr);
endmodule
```

6.6 HDL for Registers and Counters (6/12)

Shift Register

- HDL Example 6.2 (Universal Shift Register-Structural Model)

```
// 4x1 multiplexer          // behavioral model
module Mux_4x1 (mux_out, i0, i1, i2, i3, select);
  output      mux_out;
  input       i0, i1, i2, i3;
  input [1: 0] select;
  reg        mux_out;
  always @ (select, i0, i1, i2, i3)
    case (select)
      2'b00:    mux_out = i0;
      2'b01:    mux_out = i1;
      2'b10:    mux_out = i2;
      2'b11:    mux_out = i3;
    endcase
endmodule
```

```
// Behavioral model of D flip-flop
module D_flip_flop (Q, D, CLK, Clr);
  output  Q;
  input   D, CLK, Clr;
  reg     Q;
  always @ (posedge CLK, posedge Clr)
    if (Clr) Q <= 1'b0; else Q <= D;
endmodule
```

6.6 HDL for Registers and Counters (7/12)

Synchronous Counter

HDL Example 6.3 (Synchronous Counter)

```
// Four-bit binary counter with parallel load (V2001, 2005)
// See Figure 6.14 and Table 6.6
module Binary_Counter_4_Par_Load (
    output reg [3: 0]      A_count,      // Data output
    output                C_out,        // Output carry
    input [3: 0]          Data_in,      // Data input
    input                 Count,        // Active high to count
                                Load,    // Active high to load
                                CLK,      // Positive-edge sensitive
                                Clear_b   // Active low
);
assign C_out = Count && (~Load) && (A_count == 4'b1111);
always @ (posedge CLK, negedge Clear_b)
    if (~Clear_b)      A_count <= 4'b0000;
    else if (Load)      A_count <= Data_in;
    else if (Count)    A_count <= A_count + 1'b1;
    else               A_count <= A_count; // redundant statement
endmodule
```


6.6 HDL for Registers and Counters (8/12)

Ripple Counter

HDL Example 6.4 (Ripple Counter)

```
// Ripple counter (See Fig. 6.8(b))
'timescale 1ns / 100 ps
module Ripple_Counter_4bit (A3, A2, A1, A0, Count, Reset);
    output A3, A2, A1, A0;
    input Count, Reset;
    // Instantiate complementing flip-flop
    Comp_D_flip_flop F0 (A0, Count, Reset);
    Comp_D_flip_flop F1 (A1, A0, Reset);
    Comp_D_flip_flop F2 (A2, A1, Reset);
    Comp_D_flip_flop F3 (A3, A2, Reset);
endmodule
// Complementing flip-flop with delay
// Input to D flip-flop = Q'
module Comp_D_flip_flop (Q, CLK, Reset);
    output Q;
    input CLK, Reset;
    reg Q;
    always @ (negedge CLK, posedge Reset)
    if (Reset) Q <= 1'b0;
    else Q <= #2 ~Q;           // intra-assignment delay
```


6.6 HDL for Registers and Counters (9/12)

Ripple Counter

```

endmodule
// Stimulus for testing ripple counter
module t_Ripple_Counter_4bit;
    reg      Count;
    reg      Reset;
    wire     A0, A1, A2, A3;
// Instantiate ripple counter
    Ripple_Counter_4bit M0 (A3, A2, A1, A0, Count, Reset);
    always
    #5 Count = ~Count;
    initial
        begin
            Count = 1'b0;
            Reset = 1'b1;
            #4 Reset = 1'b0;
        end

    initial #170 $finish;

endmodule

```

6.6 HDL for Registers and Counters (10/12)

Ripple Counter

- **Practice Exercise 6.3 – Verilog** The bits of a four-bit ripple counter are labelled A3, A2, A1, and A0. If the flip-flops of the counter are instantiated and interconnected as shown in the text below, the counter fails to function correctly. Find the error in the code

Comp_D_flip_flop F0 (A0, Count, Reset);

Comp_D_flip_flop F1 (A1, A0, Reset);

Comp_D_flip_flop F2 (A2, A3, Reset);


Comp_D_flip_flop F3 (A3, A1, Reset);

Answer: Flip-flops *F2* and *F3* are not clocked correctly. In *F2*, replace *A3* by *A1*. In *F3*, replace *A1* by *A2*.

6.6 HDL for Registers and Counters (11/12)

Ripple Counter

- Simulation Output of HDL Example 6.4

 


(a) From 0 to 180 ns

6.6 HDL for Registers and Counters (12/12)

Ripple Counter

- Simulation Output of HDL Example 6.4

 

(b) From 70 to 98 ns

FIGURE 6.19

Simulation output of HDL Example 6.4