
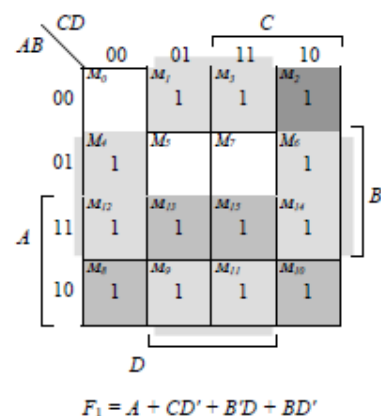
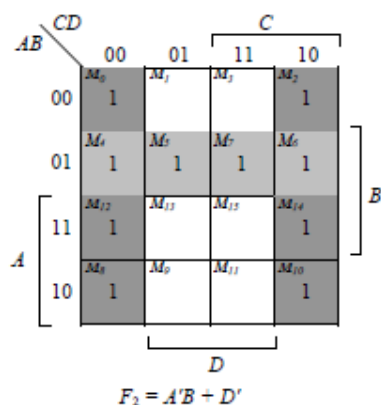




4.1

- (a) $T_1 = B'C$, $T_2 = A'B$, $T_3 = A + T_1 = A + B'C$,
 $T_4 = D \oplus T_2 = D \oplus (A'B) = A'BD' + D(A + B') = A'BD' + AD + B'D$
 $F_1 = T_3 + T_4 = A + B'C + A'BD' + AD + B'D$
 With $A + AD = A$ and $A + A'BD' = A + BD'$:
 $F_1 = A + B'C + BD' + B'D$
 Alternative cover: $F_1 = A + CD' + BD' + B'D$
- $F_2 = T_2 + D' = A'B + D'$


ABCD	T ₁	T ₂	T ₃	T ₄	F ₁	F ₂
0000	0	0	0	0	0	1
0001	0	0	0	1	1	0
0010	1	0	1	0	1	1
0011	1	0	1	1	1	0
0100	0	1	0	1	1	1
0101	0	1	0	0	0	1
0110	0	1	0	1	1	1
0111	0	1	0	0	0	1
1000	0	0	1	0	1	1
1001	0	0	1	1	1	0
1010	1	0	1	0	1	1
1011	1	0	1	1	1	0
1100	0	0	1	0	1	1
1101	0	0	1	1	1	0
1110	0	0	1	0	1	1
1111	0	0	1	1	1	0

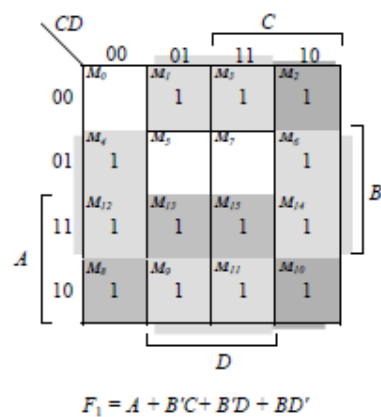

4.2

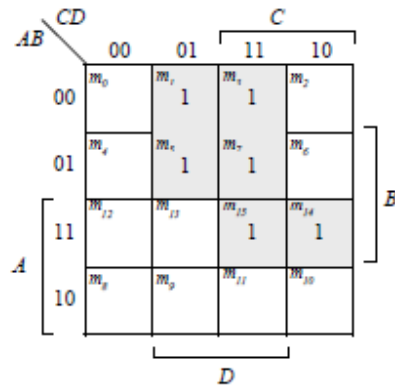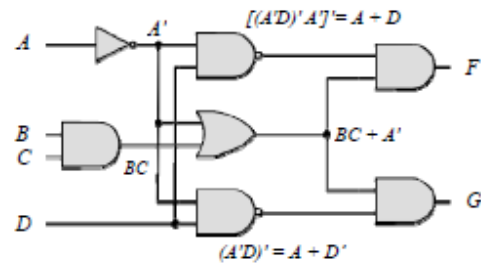

$$F = A'D + ABC + BCD = A'D + ABC$$

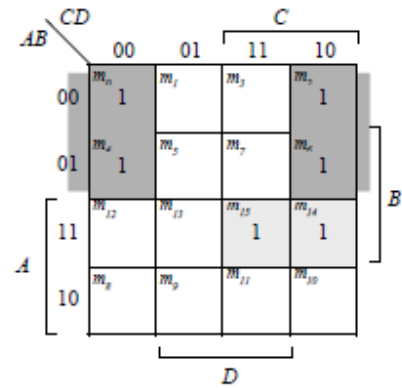

$$G = A'D' + ABC + BCD' = A'D' + ABC$$

4.3 (a) $Y_i = (A_i S' + B_i S) E'$ for $i = 0, 1, 2, 3$

(b) 1024 rows and 14 columns

4.4 (a) Circuit where output is 1 when the binary value of the inputs is more than 2. The output is 0 otherwise.

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

		y			
		00	01	11	10
x \ yz	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

$$F = x + yz$$




- (b) The output is 1 when the binary value of the inputs is not divisible by 3.

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

		y			
		00	01	11	10
x \ yz	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

$$F = x' + xy' + xz + y'z$$

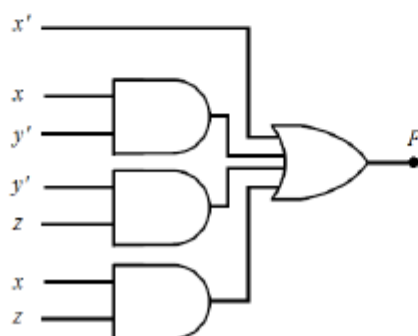


4.5

x	y	z	A	B	C
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	0	1	1
1	1	1	0	1	1

		A		y	
x	yz	00	01	11	10
		m_0	m_1	m_3	m_2
0		0	0	1	1
1		m_4	m_5	m_7	m_6
		0	0	0	0

z

$$A = x'y$$

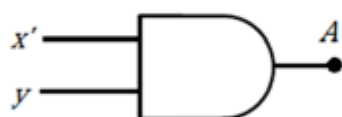


		B		y	
x	yz	00	01	11	10
		m_0	m_1	m_3	m_2
0			1	1	
1		1	1	1	1


z

$$B = x + z$$



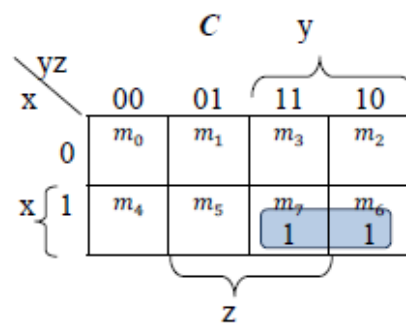


$$C = xy$$

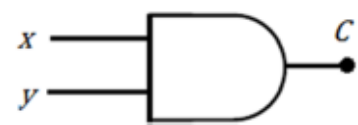


4.6 (a)

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0





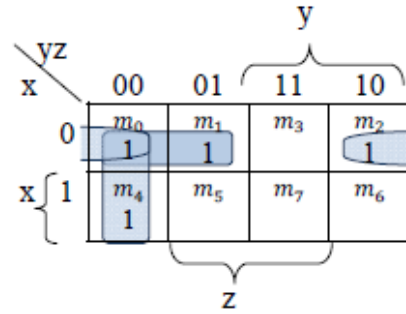


$$Y = x'y' + x'z' + y'z'$$

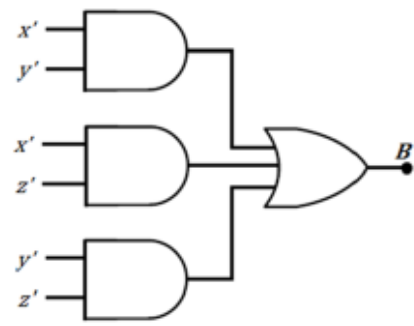


4.7 (a)

ABCD	wxyz
0000	0000
0001	0001
0011	0010
0010	0011
0110	0100
0111	0101
0101	0110
0100	0111
1100	1000
1101	1001
1111	1010
1110	1011
1010	1100
1011	1101
1001	1110
1000	1111

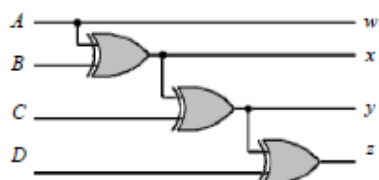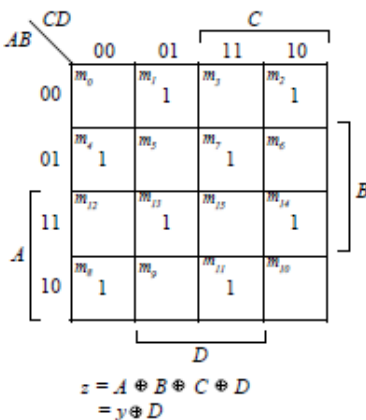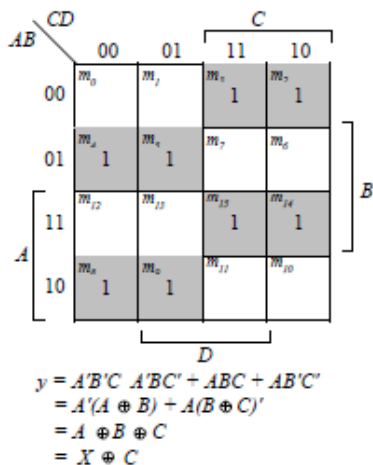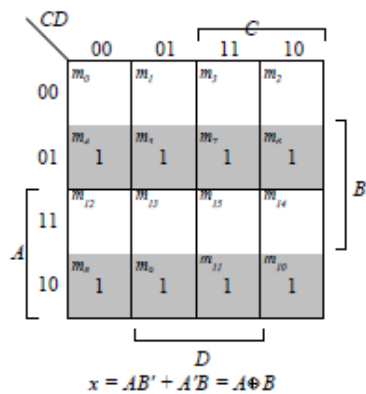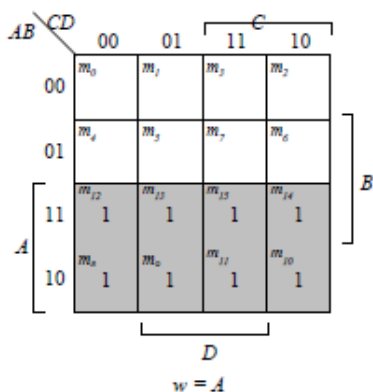


- 4.8 (a) The 8-4-2-1 code (Table 1.5) and the BCD code (Table 1.4) are identical for digits 0 – 9.

(b)

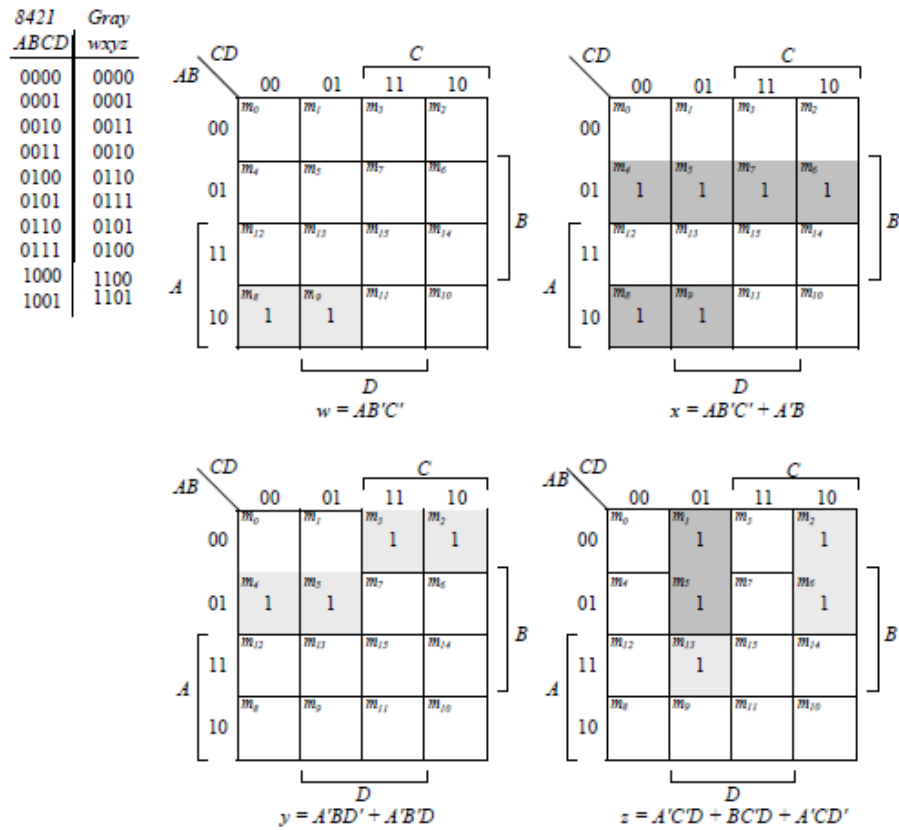


4.9


<i>ABCD</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0000	1	1	1	1	1	0	
0001	0	1	1	0	0	0	
0010	1	1	0	1	1	0	
0011	1	1	1	1	0	0	
0100	0	1	1	0	0	1	
0101	1	0	1	1	0	1	
0110	1	0	1	1	1	1	
0111	1	1	1	0	0	0	
1000	1	1	1	1	1	1	
1001	1	1	1	1	0	1	

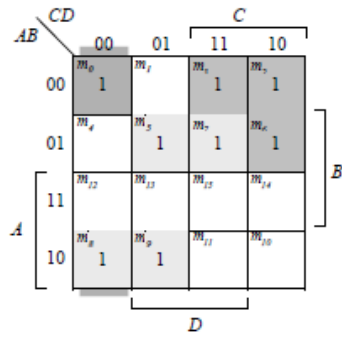


$$a = A'C + A'BD + B'C'D' + AB'C'$$

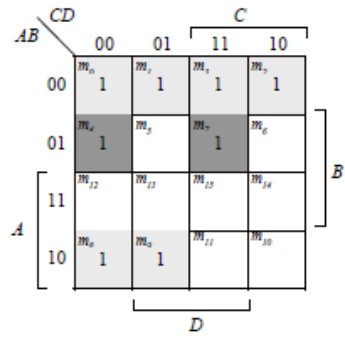


$$b = A'B' + A'C'D' + A'CD + AB'C'$$

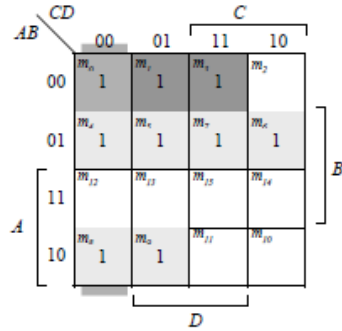


$$c = A'B + A'D + B'C'D' + AB'C'$$

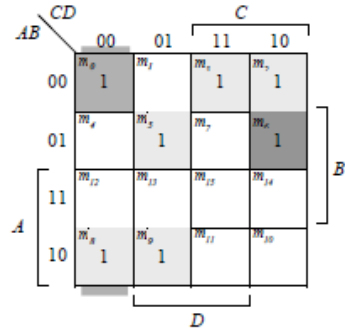

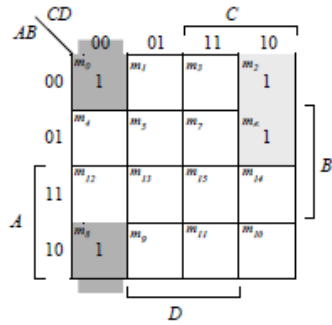
$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$



$$e = A'CD' + B'C'D'$$

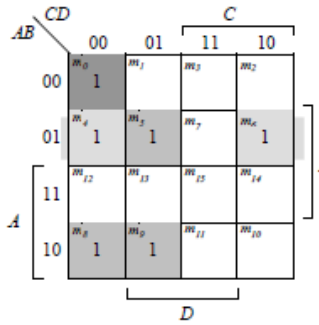


$$f = A'BC' + A'C'D' + A'BD + AB'C'$$

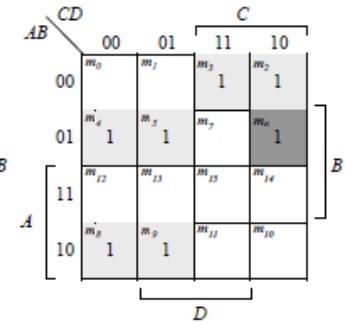


$$g = A'CD' + A'B'C + A'BC' + AB'C'$$

ABCD	wxyz
0000	0000
0001	1111
0010	1110
0011	1101
0100	1100
0101	1011
0110	1001
0111	1000
1000	1000
1001	0111
1010	0110
1011	0101
1100	0100
1101	0011
1110	0010
1111	0001

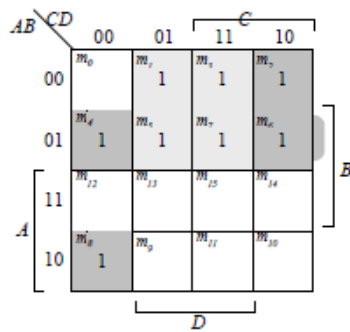


$$w = A'(B+C+D) + AB'C'D'$$

$$= A \oplus (B+C+D)$$

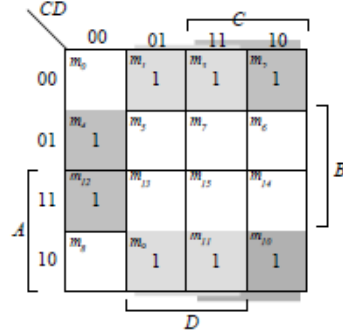


$$x = B'(C+D) + CB'D'$$

$$= B \oplus (C+D)$$

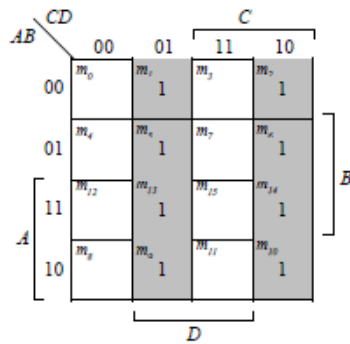

$$y = CD' + C'D = C \oplus D$$

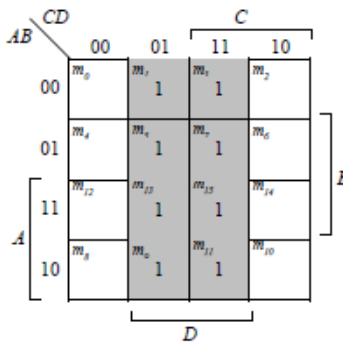


$$z = D$$

For a 5-bit 2's complementer with input E and output v:

$$v = E \oplus (A+B+C+D)$$


4.11

(a)

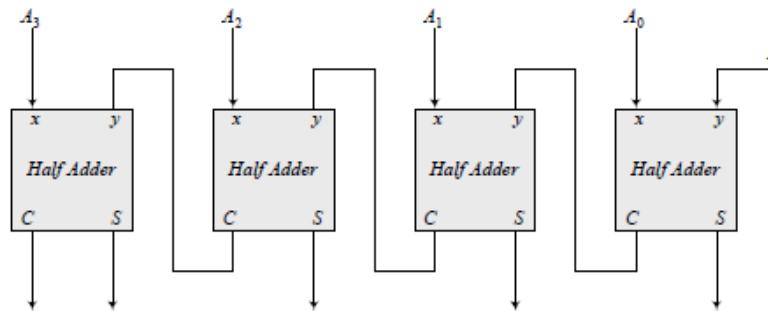

Note: 5-bit output

(b)

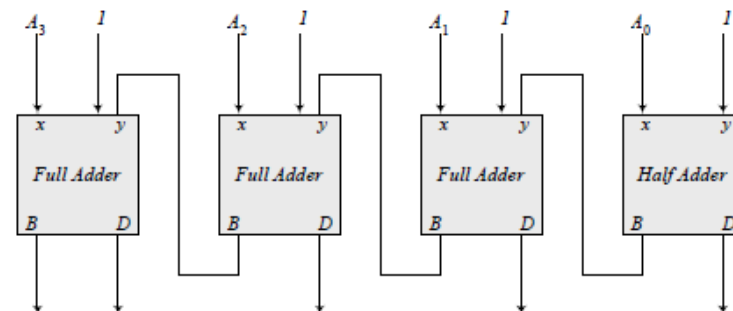

Note: To decrement the 4-bit number, add -1 to the number. In 2's complement format (add F_h) to the number. An attempt to decrement 0 will assert the borrow bit. For waveforms, see solution to Problem 4.52.

4.12

(a)

x	y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$D = x'y + xy'$$

$$B = x'y$$

(b)

x	y	z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$Diff = x \oplus y \oplus z$$

$$B_{out} = x'y + x'z + yz$$

4.13 Sum C V

(a) 1101 0 1

(b) 0001 1 1

(c) 0100 1 0

(d) 1011 0 1

(e) 1111 0 0

4.14 xor AND OR XOR

$$10 + 5 + 5 + 10 = 30 \text{ ns}$$

4.15 $C_4 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0$

4.16 (a)

$$(C_i'G_i + p_i)' = A_iB_i + (A_i + B_i)C_i = A_iB_i + A_iC_i + B_iC_i = C_{i+1}$$

$$(P_iG_i) \oplus C_i = (A_i'B_i + A_iB_i') \oplus C_i = A_i \oplus B_i \oplus C_i = S_i$$

(b)

$$\text{Output of NOR gate} = (A_0 + B_0)' = P'_0$$

$$\text{Output of NAND gate} = (A_0B_0)' = G'_0$$

$$S_1 = (P_0G'_0) \oplus C_0$$

$$C_1 = (C'_0G'_0 + P'_0)' \text{ as defined in part (a)}$$

4.17 (a)

$$(C_i'G_i + P_i)' = A_iB_i + (A_i + B_i)C_i = A_iB_i + A_iC_i + B_iC_i = C_{i+1}$$

$$(P_iG_i) \oplus C_i = (A_i'B_i + A_iB_i') \oplus C_i = A_i \oplus B_i \oplus C_i = S_i$$

(b)

$$\text{Output of NOR gate} = (A_0 + B_0)' = P'_0$$


$$\text{Output of NAND gate} = (A_0B_0)' = G'_0$$

$$S_0 = (P_0G'_0) \oplus C_0$$


$$C_1 = (C'_0G'_0 + P'_0)' \text{ as defined in part (a)}$$

Inputs $ABCD$	Outputs $wxyz$
0000	1001
0001	1000
0010	0111
0011	0110
0100	0101
0101	0100
0110	0011
0111	0010
1000	0001
1001	0000

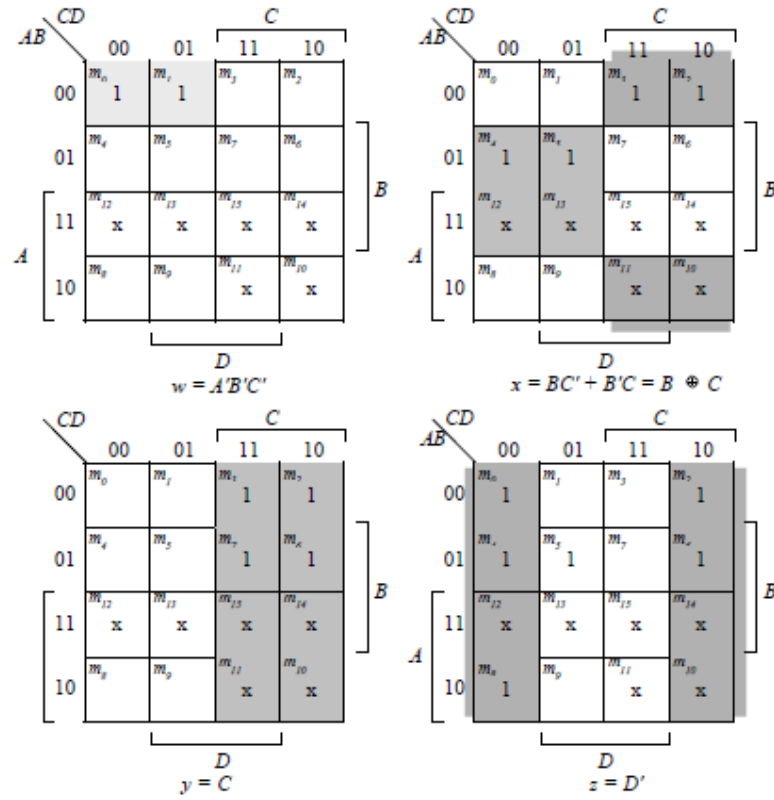
$$d(A, b, c, d) = \Sigma(10, 11, 12, 13, 14, 15)$$



4.19

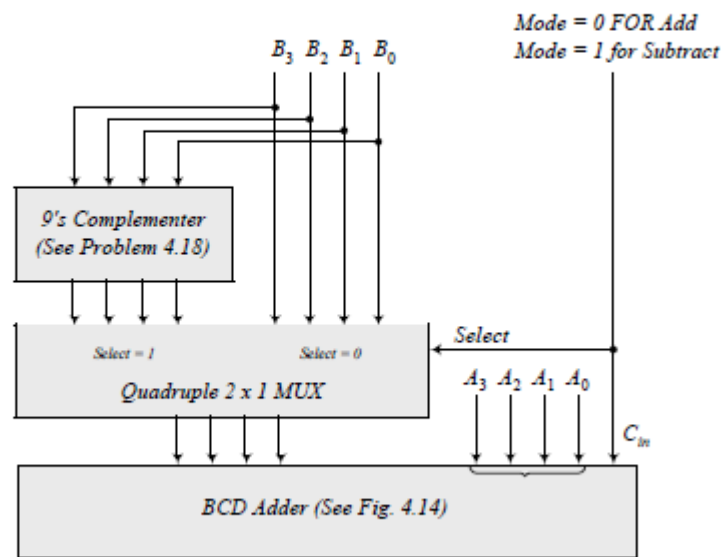

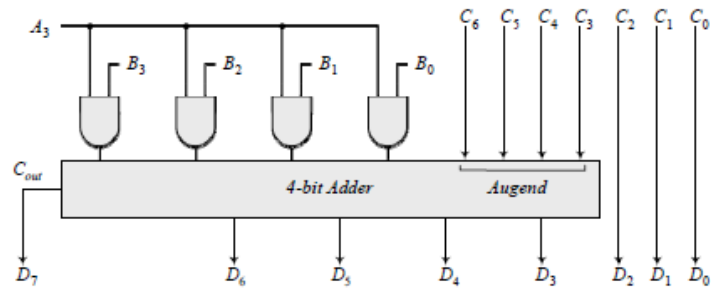4.20 Combine the following circuit with the 4-bit binary multiplier circuit of Fig. 4.16.



4.21

x_1	x_0	y_1	y_0	S_2	S_1	S_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

$y_1 y_0$		y_1				
		00	01	11	10	
$x_1 x_0$	00	m_0	m_1	m_3	m_2	x_0
	01	m_4	m_5	m_7	m_6	
	11	m_{12}	m_{13}	m_{15}	m_{14}	
	10	m_8	m_9	m_{11}	m_{10}	
		y_0				


$S_2 = x_1 x_0 y_0 + x_0 y_1 y_0 + x_1 y_1$

		y_1			
		$y_1 y_0$	00	01	$\overbrace{11 \quad 10}^{y_0}$
x_1	$x_1 x_0$	00	m_0	m_1	$\overbrace{m_3 \quad m_2}^{y_0}$
	01	m_4	$\overbrace{m_5}^{y_0}$	m_7	$\overbrace{m_6}^{y_0}$
	11	$\overbrace{m_{12}}^{y_0}$	m_{13}	$\overbrace{m_{15}}^{y_0}$	m_{14}
	10	$\overbrace{m_8 \quad m_9}^{y_0}$	m_{11}	m_{10}	

$$\begin{aligned}
 S_1 = & x_1 x_0' y_1' + x_1 x_0' y_1 \\
 & + x_1' x_0' y_1 \\
 & + x_1' y_1 y_0' \\
 & + x_1' x_0 y_1' y_0 \\
 & + x_1 x_0 y_1 y_0
 \end{aligned}$$

		y_1			
		$y_1 y_0$	00	01	$\overbrace{11 \quad 10}^{y_0}$
x_1	$x_1 x_0$	00	m_0	$\overbrace{m_1 \quad m_3}^{y_0}$	m_2
	01	$\overbrace{m_4}^{y_0}$	m_5	m_7	$\overbrace{m_6}^{y_0}$
	11	$\overbrace{m_{12}}^{y_0}$	m_{13}	m_{15}	$\overbrace{m_{14}}^{y_0}$
	10	m_8	$\overbrace{m_9 \quad m_{11}}^{y_0}$	m_{10}	

$$S_0 = x_0 y_0' + x_0' y_0$$

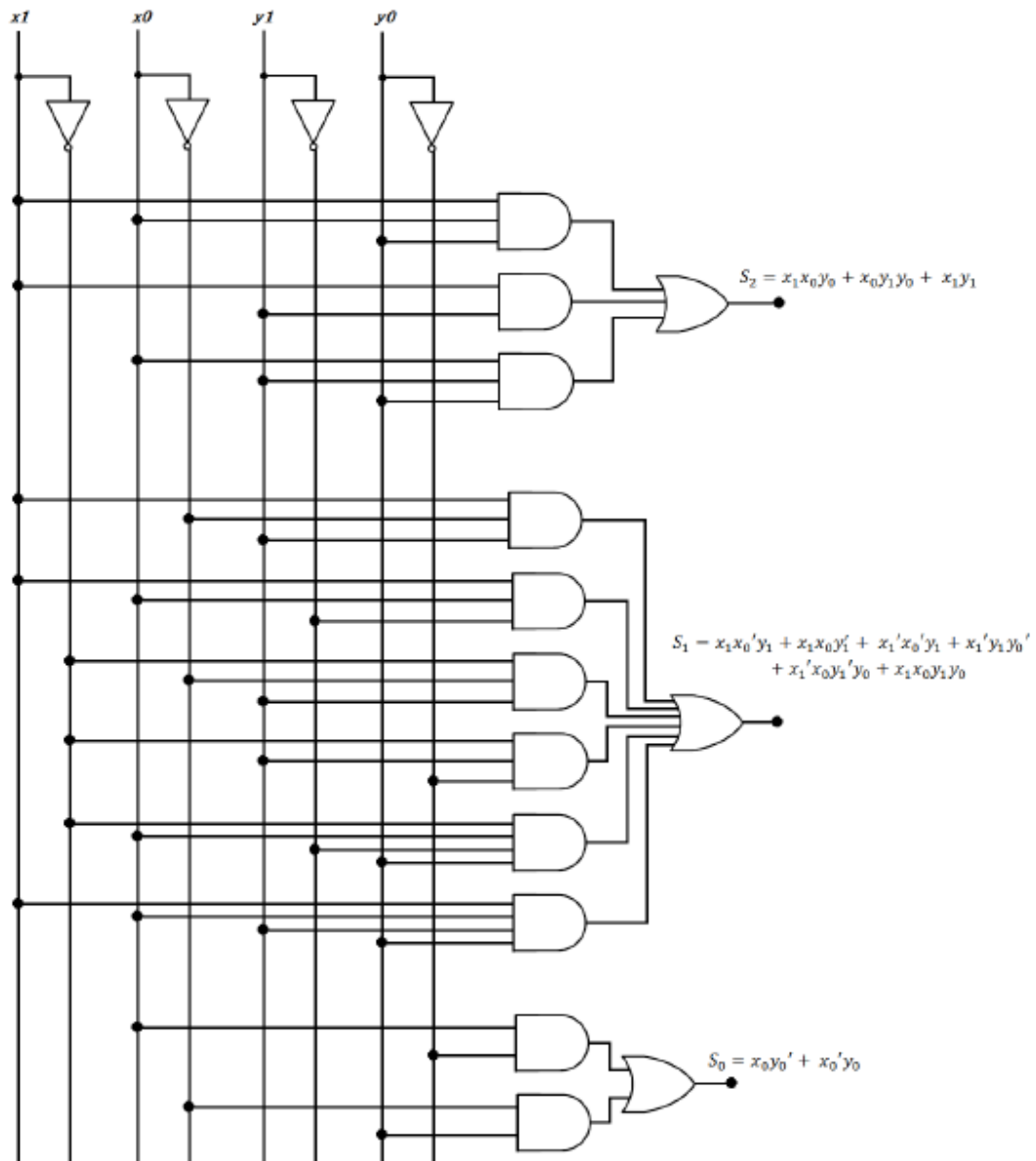

$$x = (A_0 \oplus B_0)'(A_1 \oplus B_1)'(A_2 \oplus B_2)'(A_3 \oplus B_3)'$$

4.22

XS-3 $ABCD$	Binary $wxyz$
0011	0000
0100	0001
0101	0010
0110	0011
0111	0100
1000	0101
1001	0110
1010	0111
1011	1000
1100	1001

AB \ CD		C			
		00	01	11	10
A	00	m_0 x	m_1 x	m_3	x
	01	m_4	m_5	m_7	m_6
	11	m_{12} 1	m_{13} x	m_{15} x	m_{14} x
	10	m_8	m_9	m_{11} 1	m_{10}
		D			


$w = AB + ACD$

AB \ CD		C			
		00	01	11	10
A	00	m_0 X	m_1 X	m_3	m_2 X
	01	m_4	m_5	m_7 1	m_6
	11	m_{12}	m_{13} x	m_{15} x	m_{14} x
	10	m_8 1	m_9 1	m_{11}	m_{10} 1
		D			

$x = B'C' + B'D' + BCD$
 $y = C'D + CD'$
 $z = D'$

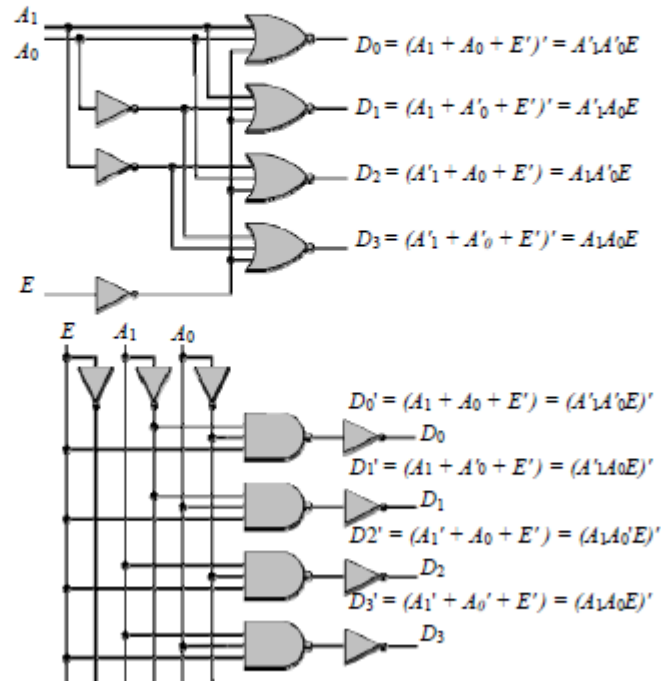4.23

$$\begin{aligned}
 D_0 &= A_1'A_0' = (A_1 + A_0)' \text{ (NOR)} & D_0' &= (A_1'A_0')' \text{ (NAND)} \\
 D_1 &= A_1'A_0 = (A_1 + A_0')' \text{ (NOR)} & D_1' &= (A_1'A_0)' \text{ (NAND)} \\
 D_2 &= A_1A_0' = (A_1' + A_0)' \text{ (NOR)} & D_2' &= (A_1A_0')' \text{ (NAND)} \\
 D_3 &= A_1A_0 = (A_1' + A_0')' \text{ (NOR)} & D_3' &= (A_1A_0)' \text{ (NAND)}
 \end{aligned}$$



4.24

Inputs: A, B, C, D

$$D_0 = A'B'C'D'$$

$$D_1 = A'B'C'D$$

$$D_2 = B'C'D'$$

$$D_3 = B'C'D$$

$$D_4 = BC'D'$$

Outputs: $D_0, D_1, \dots, D_9$

$$D_5 = BC'D$$

$$D_6 = BCD'$$


$$D_7 = BCD$$

$$D_8 = AD'$$


$$D_9 = AD$$

		C			
		00	01	11	10
AB	00	m_0 D_0	m_1 D_1	m_3 D_3	m_2 D_2
	01	m_4 D_4	m_5 D_5	m_7 D_7	m_6 D_6
	11	m_{12} x	m_{13} x	m_{15} x	m_{14} x
	10	m_8 D_8	m_9 D_9	m_{11} x	m_{10} x


4.25

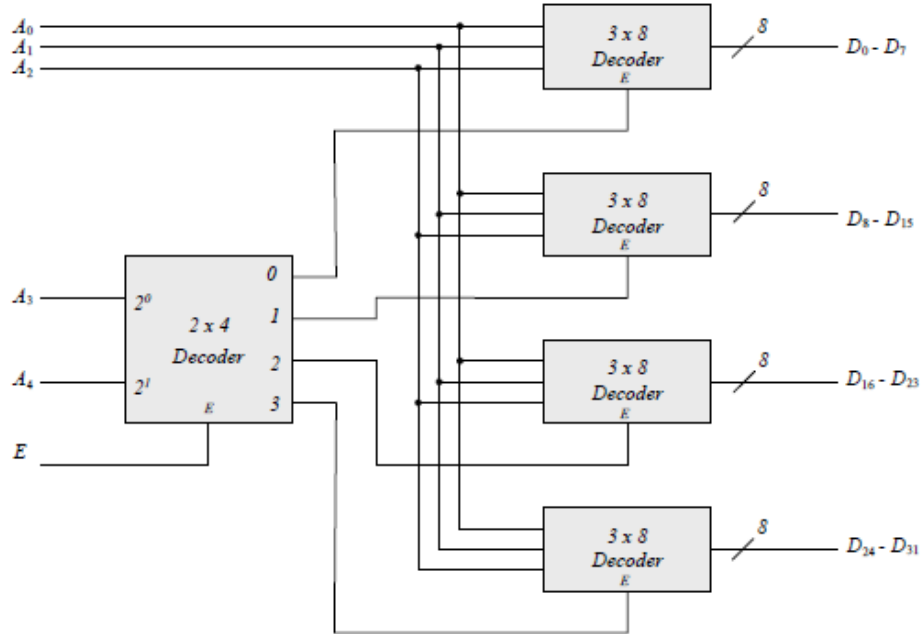

4.26

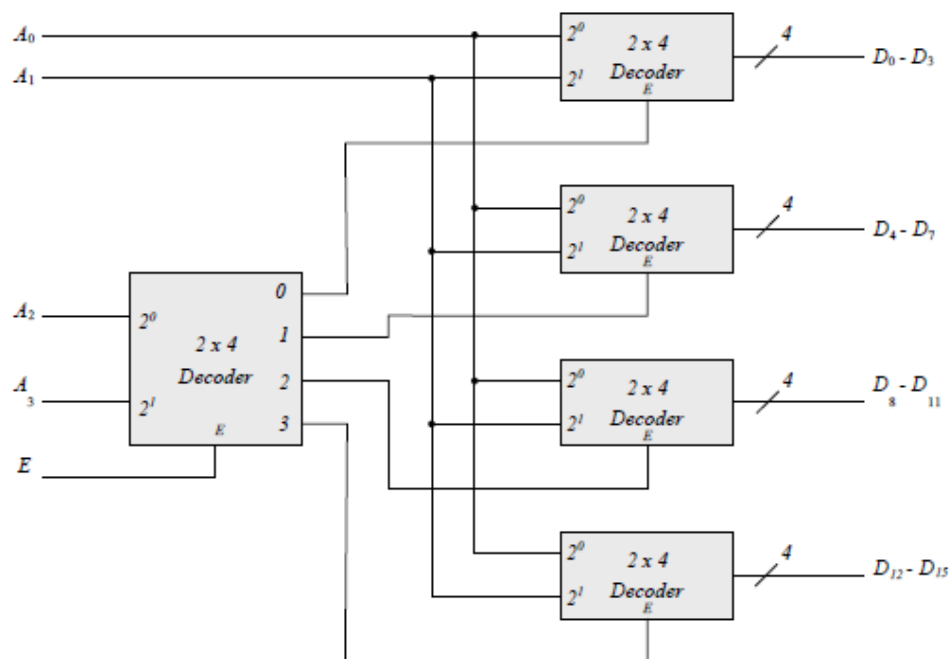

4.27

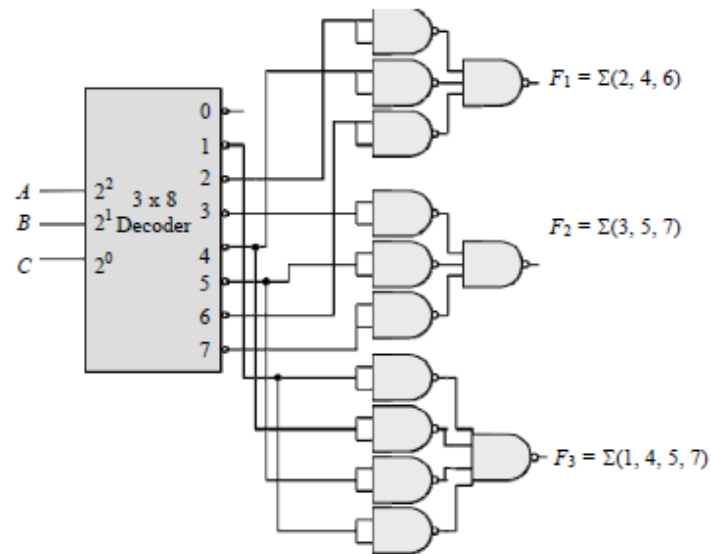


4.28 (a)


$$F_1 = x'y' + xz = x'y'z' + x'y'z + xy'z + xyz = \Sigma(0,1,5,7)$$

$$F_2 = xy'z' + yz = xy'z' + x'yz + xyz = \Sigma(3,4,7)$$
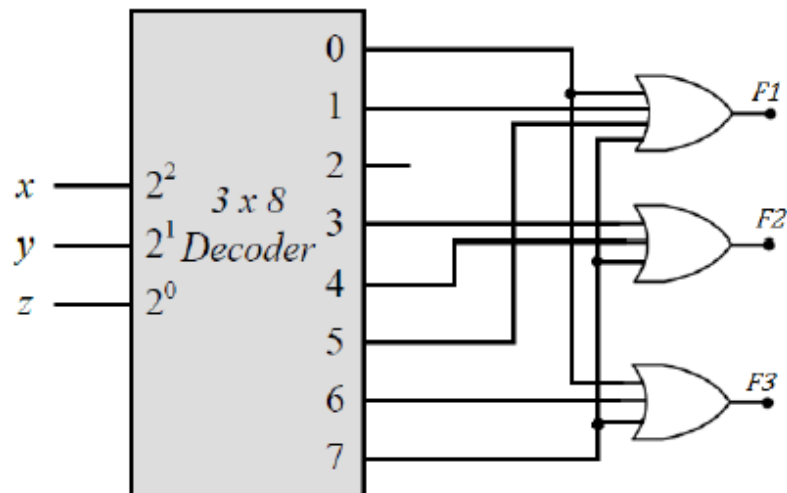
$$F_3 = x'y'z' + xy = x'y'z' + xyz' + xyz = \Sigma(0,6,7)$$



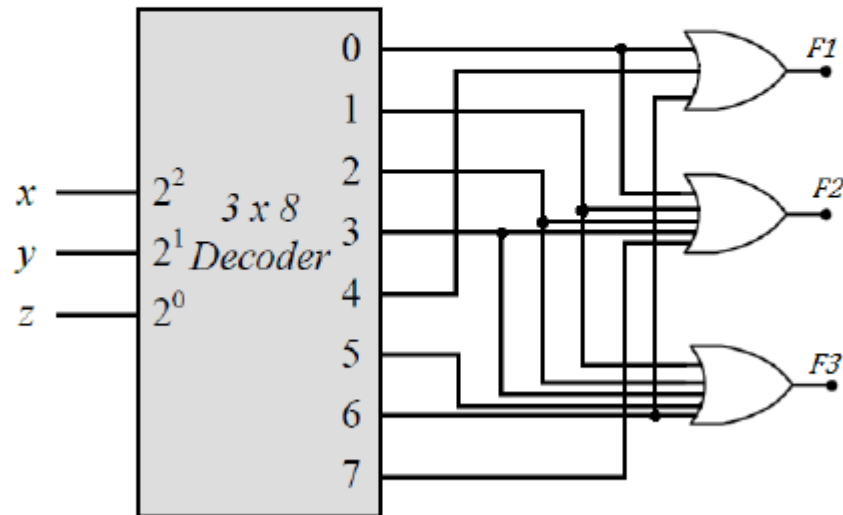- (b) $F_1 = (x + y')z' = xz' + y'z' = xyz' + xy'z' + x'y'z' = \Sigma(0,4,6)$
 $F_2 = (x' + y)(x' + z) = x' + x'z + x'y + yz = x' + yz$
 $= x'y'z' + x'y'z + x'yz' + x'yz + xyz = \Sigma(0,1,2,3,7)$
 $F_3 = (y + z)(x' + z') = x'y + yz' + x'z$
 $= x'yz' + x'yz + xyz' + x'yz' + x'y'z + x'yz = \Sigma(1,2,3,6)$



Inputs				Outputs		
D_3	D_2	D_1	D_0	x	y	V
0	0	0	0	x	x	0
x	x	x	1	0	0	1
x	x	1	0	0	1	1
x	1	0	0	1	0	1
1	0	0	0	1	1	1

D_3D_2		D_1D_0		D_1		
		00	01	11	10	
D_3	00	m_0	m_1	m_3	m_2	D_2
	01	m_4	m_5	m_7	m_6	
	11	m_{12}	m_{13}	m_{15}	m_{14}	
	10	m_8	m_9	m_{11}	m_{10}	
		D_0				


$$V = D_0 + D_1 + D_2 + D_3$$

D_3D_2		D_1D_0				
		00	01	11	10	
D_3	00	m_0 x	m_1	m_3	m_2	D_2
	01	m_4 1	m_5	m_7	m_6	
	11	m_{12} 1	m_{13}	m_{15}	m_{14}	
	10	m_8 1	m_9	m_{11}	m_{10}	
		D_0				

$$x = D_1'D_0'$$

D_3D_2		D_1D_0		D_1				
		00	01	11		10		
D_3	00	m_0	m_1	m_3	m_2			D_2
	01	m_4	m_5	m_7	m_6			
	11	m_{12}	m_{13}	m_{15}	m_{14}			
	10	m_8	m_9	m_{11}	m_{10}			
		D_0						

$$y = D_0'D_2' + D_1D_0'$$

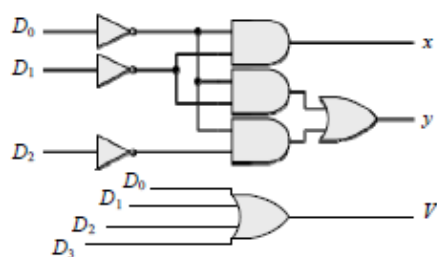


4.30


Inputs									Outputs			
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7		x	y	z	V
0	0	0	0	0	0	0	0		x	x	x	0
1	0	0	0	0	0	0	0		0	0	0	1
x	1	0	0	0	0	0	0		0	0	1	1
x	x	1	0	0	0	0	0		0	1	0	1
x	x	x	1	0	0	0	0		0	1	1	1
x	x	x	x	1	0	0	0		1	0	0	1
x	x	x	x	x	1	0	0		1	0	1	1
x	x	x	x	x	x	1	0		1	0	0	1
x	x	x	x	x	x	x	1		1	1	1	1

If $D_2 = 1, D_6 = 1$, all others = 0
Output $xyz = 100$ and $V = 1$


4.31

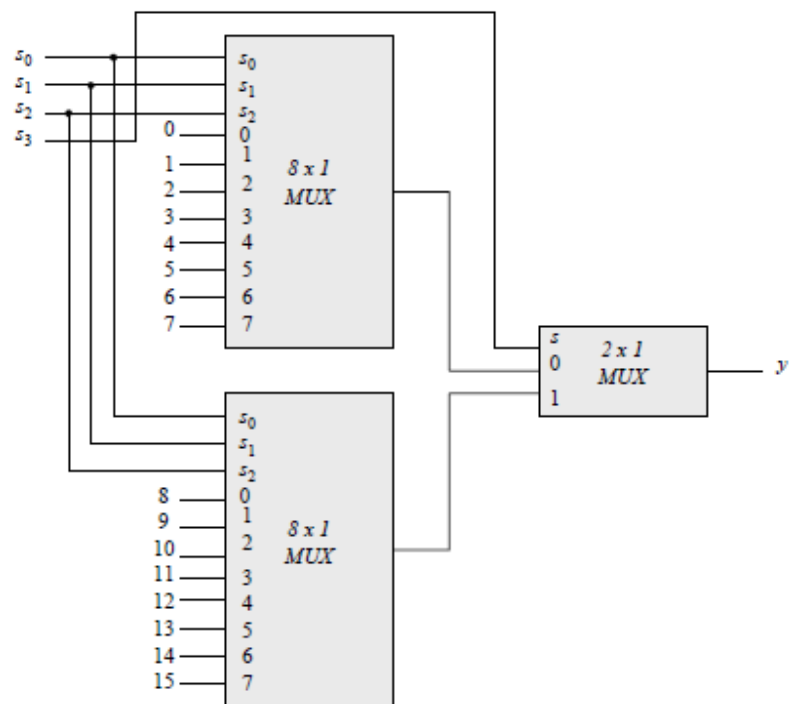

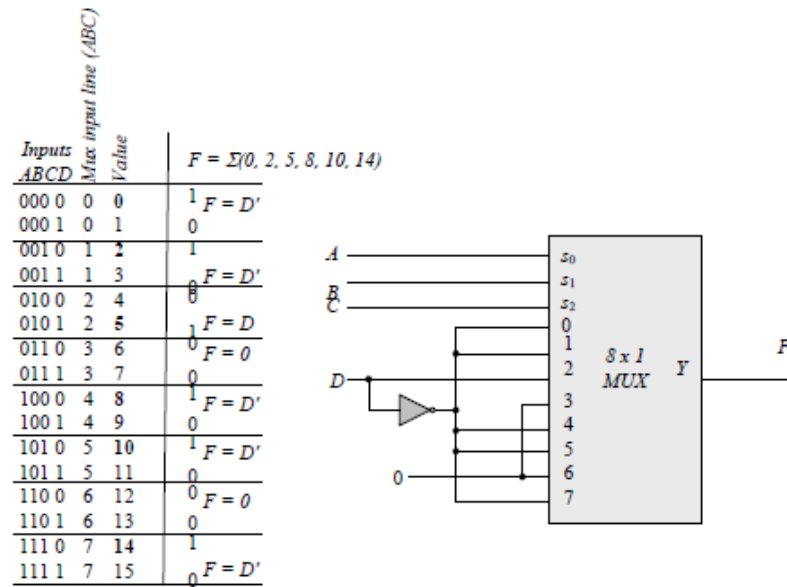4.32 (a) $F = \Sigma(0, 2, 5, 8, 10, 14)$



(b)

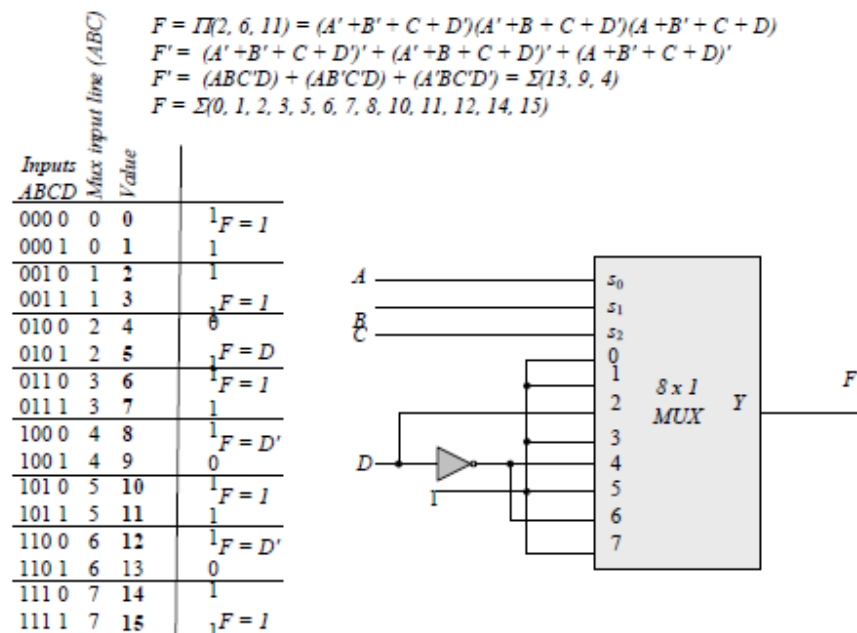

4.33 Truth Table of a Full Subtractor:

Inputs			Outputs	
x	y	B_{in}	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


x : Minuend, y : subtrahend, B_{in} : Borrow In, D : Difference, B_{out} : Borrow Out

$$D(x, y, B_{in}) = \Sigma(1, 2, 4, 7)$$

$$B_{out}(x, y, B_{in}) = \Sigma(1, 2, 3, 7)$$

D	I_0	I_1	I_2	I_3
x'	0	①	②	3
x	④	5	6	⑦
	x	x'	x'	x


B_{out}	I_0	I_1	I_2	I_3
x'	0	①	②	③
x	4	5	6	⑦
	0	x'	x'	1

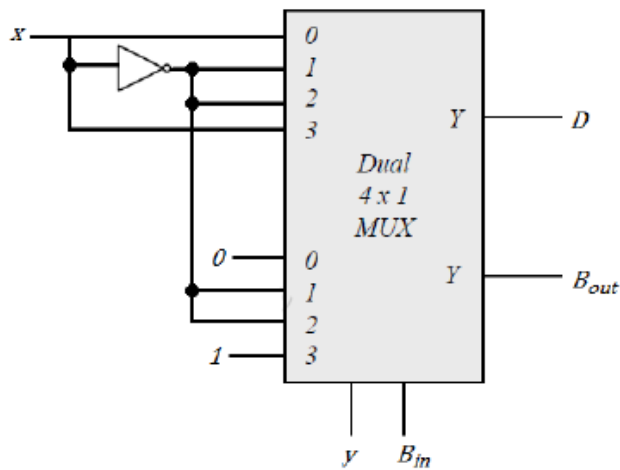

4.34 (a)

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>I</i>	<i>F</i>
0	0	0	0	$I_0 = D$	0
0	0	0	1		1
0	0	1	0	$I_1 = 0$	0
0	0	1	1		0
0	1	0	0	$I_2 = 1$	1
0	1	0	1		1
0	1	1	0	$I_3 = D'$	1
0	1	1	1		0
1	0	0	0	$I_4 = D$	0
1	0	0	1		1
1	0	1	0	$I_5 = 1$	1
1	0	1	1		1
1	1	0	0	$I_6 = 1$	1
1	1	0	1		1
1	1	1	0	$I_7 = 0$	0
1	1	1	1		0

$$F = \Sigma(1,4,5,6,9,10,11,12,13)$$

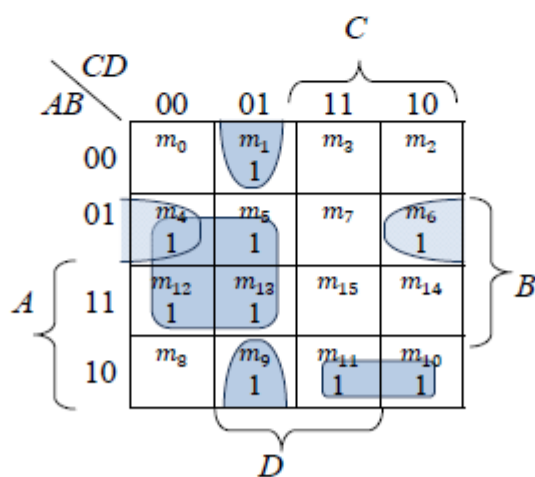


$$F = A'BD' + AB'C + B'C'D + BC'$$

(b)


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>I</i>	<i>F</i>
0	0	0	0	$I_0 = D$	0
0	0	0	1		1
0	0	1	0	$I_1 = D$	0
0	0	1	1		1
0	1	0	0	$I_2 = 0$	0
0	1	0	1		0
0	1	1	0	$I_3 = 0$	0
0	1	1	1		0
1	0	0	0	$I_4 = D'$	1
1	0	0	1		0
1	0	1	0	$I_5 = 1$	1
1	0	1	1		1
1	1	0	0	$I_6 = 0$	0
1	1	0	1		0
1	1	1	0	$I_7 = D'$	1
1	1	1	1		0

$$F = \Sigma(1,3,8,10,11,14)$$

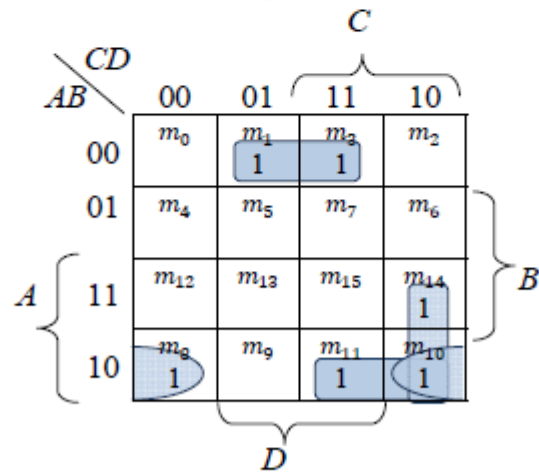


$$F = A'B'D + AB'D' + AB'C + ACD'$$


4.35 (a)

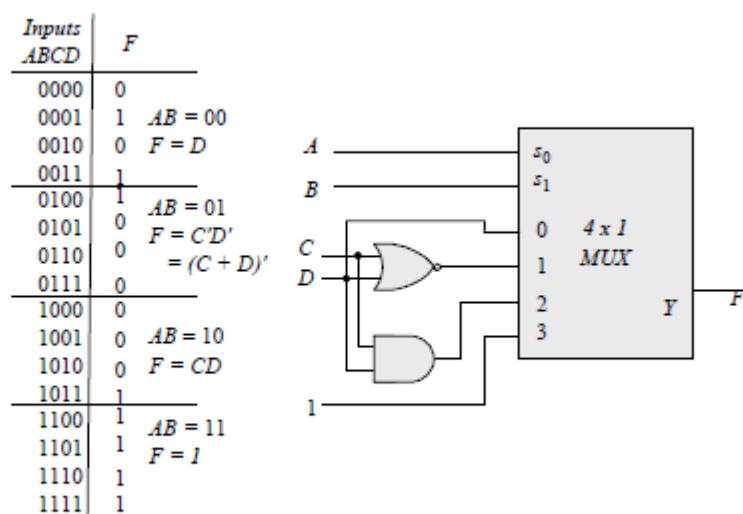

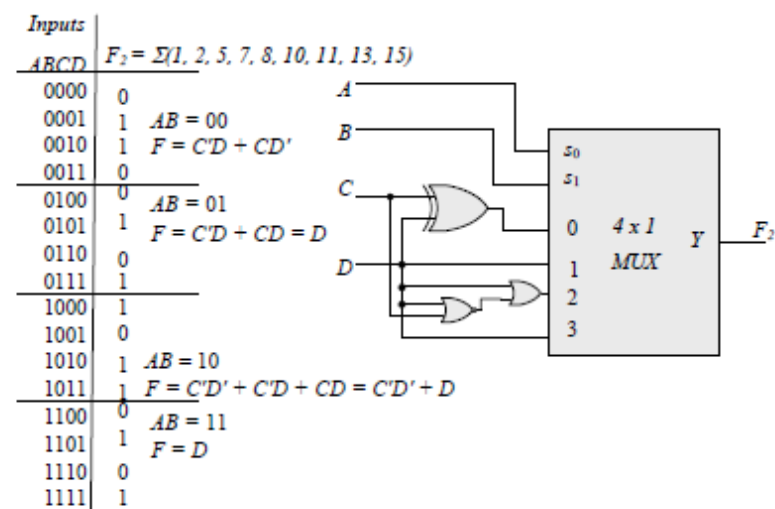(b) $F = \Sigma(1, 2, 5, 7, 8, 10, 11, 13, 15)$



4.63

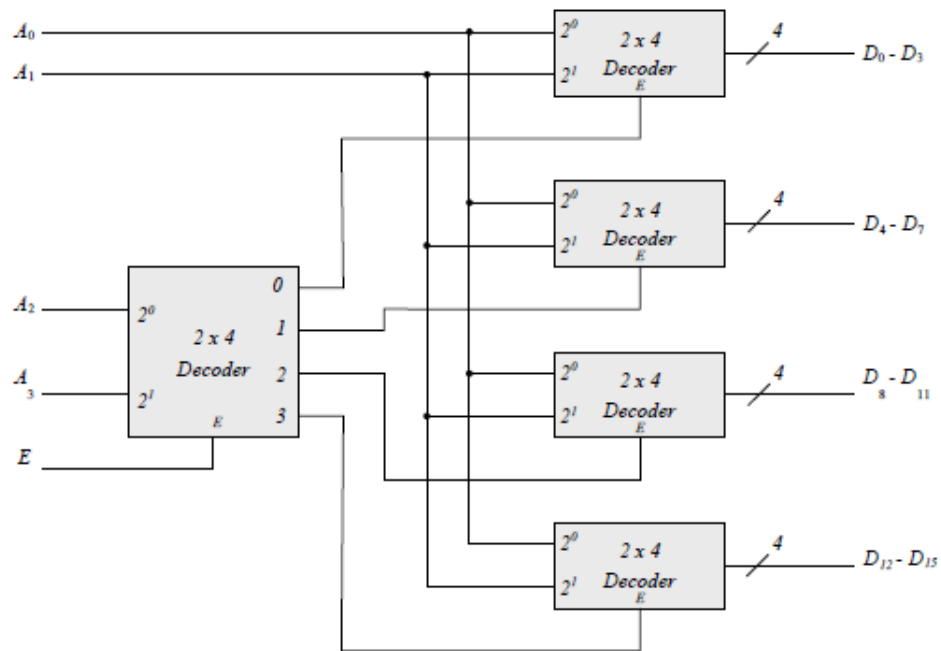

4.64

Inputs									Outputs			
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7		x	y	z	V
0	0	0	0	0	0	0	0		x	x	x	0
1	0	0	0	0	0	0	0		0	0	0	1
x	1	0	0	0	0	0	0		0	0	1	1
x	x	1	0	0	0	0	0		0	1	0	1
x	x	x	1	0	0	0	0		0	1	1	1
x	x	x	x	1	0	0	0		1	0	0	1
x	x	x	x	x	1	0	0		1	0	1	1
x	x	x	x	x	x	1	0		1	0	0	1
x	x	x	x	x	x	x	1		1	1	1	1

If $D_2 = 1$, $D_6 = 1$, all others = 0
Output $xyz = 100$ and $V = 1$

4.65

